

ECEN 429: Introduction to Digital Systems Design Laboratory

North Carolina Agricultural and Technical State University

Department of Electrical and Computer Engineering

Ian Parker (Reporter)

Tayanna Lee (Lab Partner)


April 4, 2019

Lab #8


Introduction:

For this lab, we learn how to create a counter with multiple functionalities. We display how the counter changes from one function to the next by implementing a finite state machine. Finally, after combining both into a top-level design, we make sure to display the results on the Seven-Segment Display.

Part 1 Finite State Machine

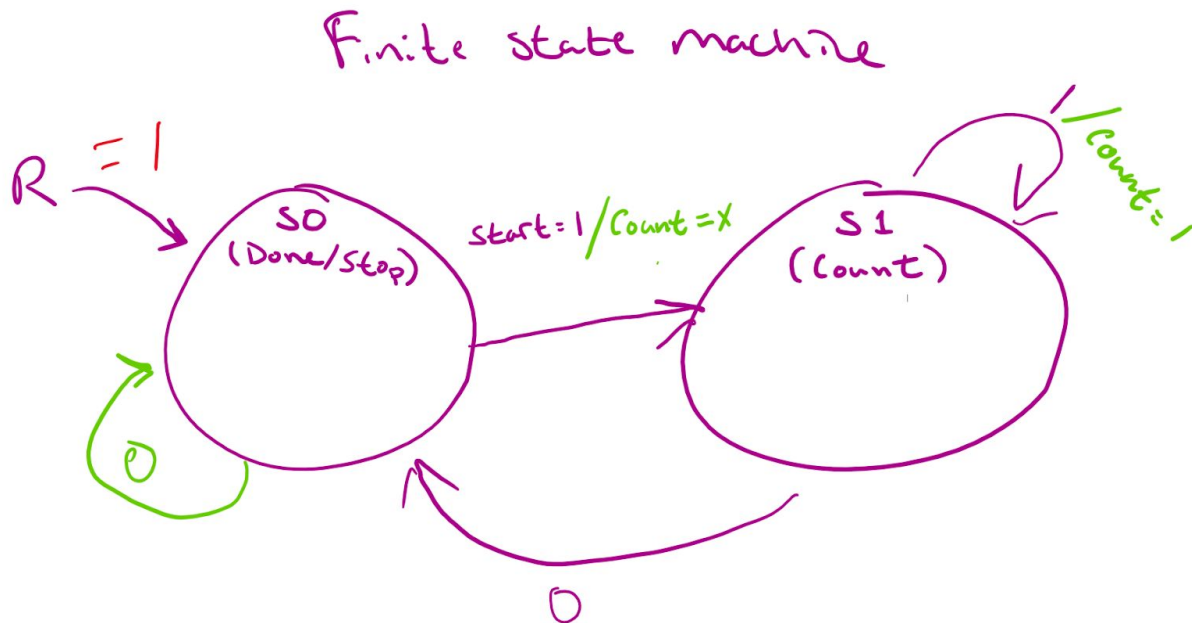

Schematic

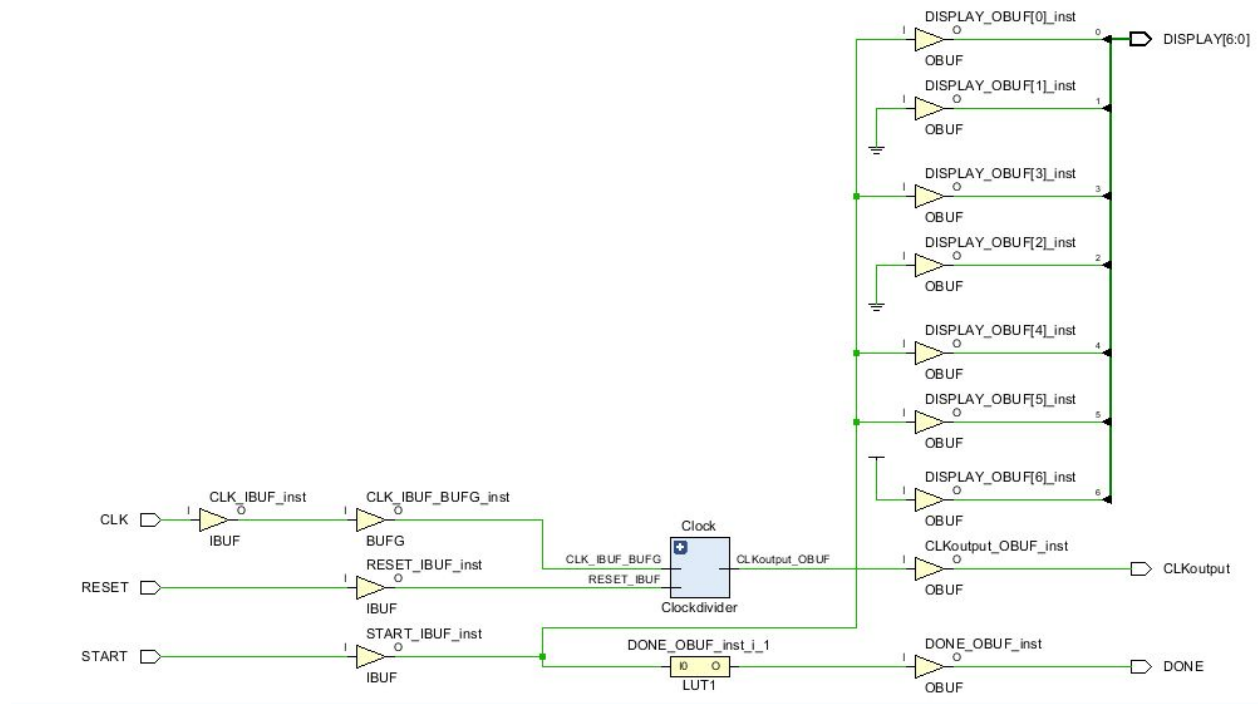

PIN ASSIGNMENTS

All ports (12)									
DISPLAY (7)									
OUT							<input checked="" type="checkbox"/>	34	LVC MOS33*
DISPLAY[6]	OUT				U7	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	34	LVC MOS33*
DISPLAY[5]	OUT				V5	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	34	LVC MOS33*
DISPLAY[4]	OUT				U5	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	34	LVC MOS33*
DISPLAY[3]	OUT				V8	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	34	LVC MOS33*
DISPLAY[2]	OUT				U8	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	34	LVC MOS33*
DISPLAY[1]	OUT				W6	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	34	LVC MOS33*
DISPLAY[0]	OUT				W7	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	34	LVC MOS33*
Scalar ports (5)									
CLK	IN				W5	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	34	LVC MOS33*
CLKoutput	OUT				V3	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	34	LVC MOS33*
DONE	OUT				L1	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	35	LVC MOS33*
RESET	IN				T1	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	34	LVC MOS33*
START	IN				R2	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	34	LVC MOS33*

Figure 1.1) Low Clock. State 0


 



Figure 1.2) High Clock. State 1

Part 2
Finite State Machine

Finite state machine

 

Schematic

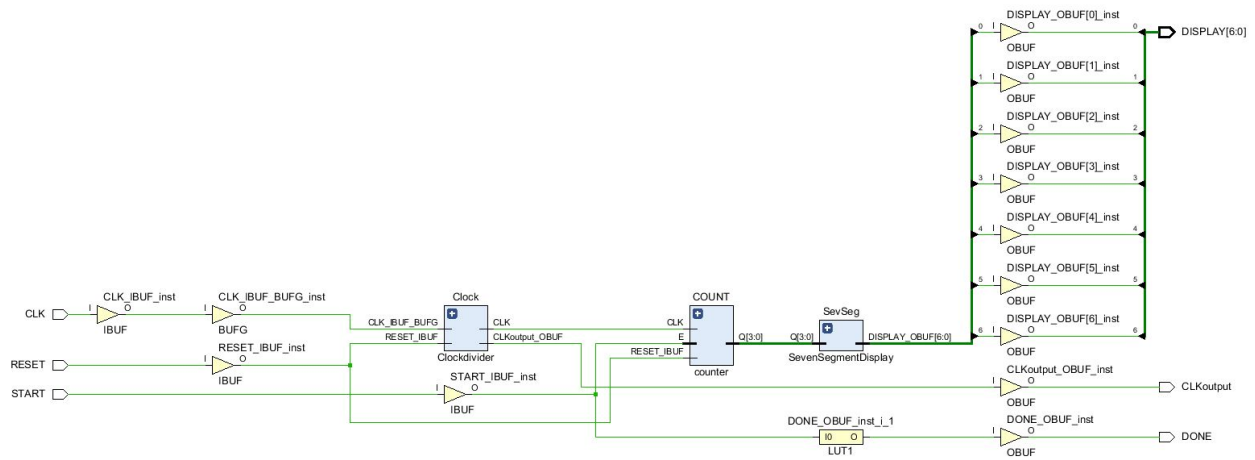

PIN ASSIGNMENTS

All ports (12)									
DISPLAY (7)	OUT						<input checked="" type="checkbox"/>	34	LVC MOS33*
DISPLAY[6]	OUT				U7	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	34	LVC MOS33*
DISPLAY[5]	OUT				V5	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	34	LVC MOS33*
DISPLAY[4]	OUT				U5	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	34	LVC MOS33*
DISPLAY[3]	OUT				V8	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	34	LVC MOS33*
DISPLAY[2]	OUT				U8	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	34	LVC MOS33*
DISPLAY[1]	OUT				W6	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	34	LVC MOS33*
DISPLAY[0]	OUT				W7	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	34	LVC MOS33*
Scalar ports (5)									
CLK	IN				W5	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	34	LVC MOS33*
CLKoutput	OUT				V3	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	34	LVC MOS33*
DONE	OUT				L1	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	35	LVC MOS33*
RESET	IN				T1	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	34	LVC MOS33*
START	IN				R2	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	34	LVC MOS33*

Results

 


Figure 2.1) High Clock. The count is at 7

 


Figure 2.1) High Clock. The count is at F or 15 in HEX

Conclusion:

In conclusion, this continues to strengthen our use of components and understanding of FSM, and how they can be used as a control unit (in this case the counter). The previous lab was very difficult and gave us a cushion for this lab and labs to come, when it comes to implementing FSMs.

PART 1 VHDL CODE

CLOCK DIVIDER

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use ieee.std_logic_unsigned.all;

entity Clockdivider is
Port ( CLK : in  STD_LOGIC;
      RESET : in  STD_LOGIC;
      SlowClock,ledO : out  STD_LOGIC);
end Clockdivider;

architecture behavioral of Clockdivider is
signal slowSig: std_logic;
begin
    process
        variable cnt :  std_logic_vector(26 downto 0):= "0000000000000000000000000000";
        begin
            -- calculations
            wait until ((CLK'EVENT) AND (CLK = '1'));
            if (RESET = '1') then
                cnt := "0000000000000000000000000000";
            else
                cnt := cnt + 1; -- count to 26
            end if;

            SlowClock <= cnt(26);
            slowSig<=cnt(26);

            if(slowSig='1')then
                ledO<='1';
            else
                ledO<='0';
            end if;

        end process;
    end Behavioral;
```

DISPLAY

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
use ieee.std_logic_unsigned.all;
```

```
entity SevenSegmentDisplay is  
  Port (input: in std_logic_vector (3 downto 0);  
        output:out std_logic_vector(6 downto 0));-- lsb  
end SevenSegmentDisplay;
```

architecture Behavioral of SevenSegmentDisplay is

```
begin  
  process(input)  
  begin  
    case input is  
      when "0000" =>  
        output <= "1000000"; --0  
      when "0001" =>  
        output <= "1111001"; --1  
      when "0010" =>  
        output <= "0100100";--2  
      when "0011" =>  
        output <= "0110000"; --3  
      when "0100" =>  
        output <= "0011001"; --4  
      when "0101" =>  
        output <= "0010010";--5  
      when "0110" =>  
        output <= "0000010";--6  
      when "0111" =>  
        output <= "1111000";--7  
      when "1000" =>  
        output <= "0000000";--8  
      when "1001" =>  
        output <= "0010000";--9  
      when "1010" =>  
        output <= "0100000";--10 A  
      when "1011" =>  
        output <= "0000011";--11 B  
      when "1100" =>  
        output <= "1000110";--12 C
```

```

when "1101" =>
    output <= "0100001";--13 D
when "1110" =>
    output <= "0000110";--14 E
when "1111" =>
    output <= "0001110";--15 F
end case;
end process;

end Behavioral;

```

COUNTER

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use ieee.std_logic_unsigned.all;

entity counter is
    Port (CLK,R,ENABLE,CLEAR: in std_logic;
          COUNTER :out std_logic_vector(3 downto 0));
end counter;

architecture Behavioral of counter is
    signal tmp: std_logic_vector(3 downto 0);--temporary signal for counter

begin
    process(R,CLK)
    begin
        if(R='1')then
            tmp<="0000";--reset the count
        elsif(CLK'event and (CLK='1'))then
            if(ENABLE='1') then
                tmp <= tmp + "0001";--start the count
            end if;
        end if;
        COUNTER <= tmp;
    end process;
end Behavioral;

```


FSM

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use ieee.std_logic_unsigned.all;

entity FSM is
  Port (CLK,R,START: in std_logic;
        STATE : out std_logic_vector(3 downto 0);
        DONE,ENABLE,CLEAR: out std_logic);
end FSM;

architecture Behavioral of fsm is
  signal CS,NS: std_logic;
  signal STATEDISPLAYtmp : std_logic_vector(3 downto 0);
  begin
    process(CLK, R)
    begin
      if(R='1') then
        CS<='0';
        CLEAR<='1';
        --STATEDISPLAYtmp <= "0000";
      elsif(CLK' event and (CLK='1'))then
        CS<=NS;
        STATEDISPLAYtmp<= STATEDISPLAYtmp;
      end if;
    end process;
    process(CS,START)
    begin
      case CS is
        when '0' => --State 0 handles both the DONE state and the INITIAL state of the FSM
          if(START ='1') then
```

```

        NS<='1';
        ENABLE<='1';
        DONE<='0';
        STATEDISPLAYtmp <= "0001";
    elsif(START='0')then
        ENABLE<='0';
        NS<= '0';
        DONE<='1';
        STATEDISPLAYtmp <= "0000";
    end if;
when '1' => --count state
    if(START ='1') then
        NS<='1';
        ENABLE<='1';
        DONE<='0';
        STATEDISPLAYtmp <= "0000";
    elsif(START='0')then
        ENABLE<='0';
        NS<= '0';
        DONE<='1';
        STATEDISPLAYtmp <= "0001";
    end if;
end case;
end process;
STATE<= STATEDISPLAYtmp;
end Behavioral;

```

TOP LEVEL

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use ieee.std_logic_unsigned.all;

entity TopLevel is
    Port (CLK,START,RESET: in std_logic;
        CLKoutput,DONE: out std_logic;
        DISPLAY: out std_logic_vector(6 downto 0) );
end TopLevel;

architecture Behavioral of TopLevel is

    signal tmpEnable,tmpCLEAR,tmpCLK: std_logic;
    signal tmpDisplay: std_logic_vector( 3 downto 0);

```

```

component FSM Port (CLK,R,START: in std_logic;
                    DONE,ENABLE,CLEAR: out std_logic);
end component;
--ClockDivider Component Declaration
component ClockDivider Port ( clk : in  STD_LOGIC;
                             reset : in  STD_LOGIC;
                             SlowClock,ledO : out  STD_LOGIC);
end component;
--Counter Component Declaration
component Counter Port (CLK,R,ENABLE,CLEAR: in std_logic;
                        COUNTER :out std_logic_vector(3 downto 0));
end component;
--SevenSegmentDisplay Component Declaration
component SevenSegmentDisplay Port (input: in std_logic_vector (3 downto 0);
                                     output:out std_logic_vector(6 downto 0));
end component;

begin
    --Component Instantiation
    Clock: ClockDivider port
map(CLK=>CLK,RESET=>RESET,SlowClock=>tmpCLK,ledO=>CLKoutput);
    Machine: FSM port
map(CLK=>tmpCLK,R=>RESET,START=>START,DONE=>DONE,ENABLE=>tmpEnable,CLEAR=>tmpCLEAR);
    COUNT : COUNTER port
map(CLK=>tmpClk,R=>RESET,ENABLE=>tmpEnable,CLEAR=>tmpCLEAR,COUNTER=>tmpDisplay);
    SevSeg: SevenSegmentDisplay port map(input=>tmpDisplay,output=>DISPLAY);

end Behavioral;

```

CONSTRAINTS

```

set_property IOSTANDARD LVCMOS33 [get_ports {DISPLAY[6]}]
set_property IOSTANDARD LVCMOS33 [get_ports {DISPLAY[5]}]
set_property IOSTANDARD LVCMOS33 [get_ports {DISPLAY[4]}]
set_property IOSTANDARD LVCMOS33 [get_ports {DISPLAY[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {DISPLAY[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {DISPLAY[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {DISPLAY[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports CLK]
set_property IOSTANDARD LVCMOS33 [get_ports CLKoutput]

```

```

set_property IOSTANDARD LVCMOS33 [get_ports DONE]
set_property IOSTANDARD LVCMOS33 [get_ports RESET]
set_property IOSTANDARD LVCMOS33 [get_ports START]
set_property PACKAGE_PIN U7 [get_ports {DISPLAY[6]}]
set_property PACKAGE_PIN V5 [get_ports {DISPLAY[5]}]
set_property PACKAGE_PIN U5 [get_ports {DISPLAY[4]}]
set_property PACKAGE_PIN V8 [get_ports {DISPLAY[3]}]
set_property PACKAGE_PIN U8 [get_ports {DISPLAY[2]}]
set_property PACKAGE_PIN W6 [get_ports {DISPLAY[1]}]
set_property PACKAGE_PIN W7 [get_ports {DISPLAY[0]}]
set_property PACKAGE_PIN L1 [get_ports DONE]
set_property PACKAGE_PIN T1 [get_ports RESET]
set_property PACKAGE_PIN W5 [get_ports CLK]
set_property PACKAGE_PIN V3 [get_ports CLKoutput]
set_property PACKAGE_PIN R2 [get_ports START]

```

PART 2 VHDL CODE

CLOCK DIVIDER

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use ieee.std_logic_unsigned.all;

```

```

entity Clockdivider is
Port ( CLK : in  STD_LOGIC;
      RESET : in  STD_LOGIC;
      SlowClock,ledO : out  STD_LOGIC);
end Clockdivider;

```

```

architecture behavioral of Clockdivider is
signal slowSig: std_logic;
begin
    process
        variable cnt :  std_logic_vector(26 downto 0):= "00000000000000000000000000";
        begin
            -- calculations
            wait until ((CLK'EVENT) AND (CLK = '1'));
            if (RESET = '1') then
                cnt := "00000000000000000000000000";
            else
                cnt := cnt + 1; -- count to 26
            end if;

            SlowClock <= cnt(26);
        end process;
    end architecture;

```



```

        slowSig<=cnt(26);

        if(slowSig='1')then
            ledO<='1';
        else
            ledO<='0';
        end if;

    end process;
end Behavioral;

```

Display VHDL

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use ieee.std_logic_unsigned.all;

entity SevenSegmentDisplay is
    Port (input: in std_logic_vector (3 downto 0);
          output:out std_logic_vector(6 downto 0));-- lsb
end SevenSegmentDisplay;

architecture Behavioral of SevenSegmentDisplay is

begin
    process(input)
    begin
        case input is
            when "0000" =>
                output <= "1000000"; --0
            when "0001" =>
                output <= "1111001"; --1
            when "0010" =>
                output <= "0100100";--2
            when "0011" =>
                output <= "0110000"; --3
            when "0100" =>
                output <= "0011001"; --4
            when "0101" =>
                output <= "0010010";--5

```

```

when "0110" =>
    output <= "0000010";--6
when "0111" =>
    output <= "1111000";--7
when "1000" =>
    output <= "0000000";--8
when "1001" =>
    output <= "0010000";--9
when "1010" =>
    output <= "0100000";--10 A
when "1011" =>
    output <= "0000011";--11 B
when "1100" =>
    output <= "1000110";--12 C
when "1101" =>
    output <= "0100001";--13 D
when "1110" =>
    output <= "0000110";--14 E
when "1111" =>
    output <= "0001110";--15 F
end case;
end process;

end Behavioral;

```

Counter VHDL

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use ieee.std_logic_unsigned.all;

entity counter is
    Port (CLK,R,ENABLE,CLEAR: in std_logic;
          COUNTER :out std_logic_vector(3 downto 0));
end counter;

architecture Behavioral of counter is
    signal tmp: std_logic_vector(3 downto 0);--temporary signal for counter

```

```

begin
process(R,CLK)
begin
    if(R='1')then
        tmp<="0000";--reset the count
    elsif(CLK'event and (CLK='1'))then
        if(ENABLE='1') then
            tmp <= tmp + "0001";--start the count
        end if;
    end if;
    COUNTER <= tmp;
end process;
end Behavioral;

```

FSM VHDL

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use ieee.std_logic_unsigned.all;

entity FSM is
    Port (CLK,R,START: in std_logic;
          DONE,ENABLE,CLEAR: out std_logic);
end FSM;

architecture Behavioral of fsm is
    signal CS,NS: std_logic;
    begin
        process(CLK, R)
        begin
            if(R='1') then
                CS<='0';
                CLEAR<='1';
            elsif(CLK' event and (CLK='1'))then
                CS<=NS;
            end if;
        end process;
        process(CS,START)

```

```

begin
  case CS is
    when '0' => --State 0 handles both the DONE state and the INITIAL state of the FSM
      if(START ='1') then
        NS<='1';
        ENABLE<='1';
        DONE<='0';
      elsif(START='0')then
        ENABLE<='0';
        NS<= '0';
        DONE<='1';
      end if;
    when '1' => --count state
      if(START ='1') then
        NS<='1';
        ENABLE<='1';
        DONE<='0';
      elsif(START='0')then
        ENABLE<='0';
        NS<= '0';
        DONE<='1';
      end if;
    end case;
  end process;
end Behavioral;

```

TopLevel VHDL

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use ieee.std_logic_unsigned.all;

entity TopLevel is
  Port (CLK,START,RESET: in std_logic;
        CLKoutput,DONE: out std_logic;
        DISPLAY: out std_logic_vector(6 downto 0) );
end TopLevel;

```


architecture Behavioral of TopLevel is

```
signal tmpEnable,tmpCLEAR,tmpCLK: std_logic;
signal tmpDisplay: std_logic_vector( 3 downto 0);

    component FSM Port (CLK,R,START: in std_logic;
        DONE,ENABLE,CLEAR: out std_logic);
    end component;
--ClockDivider Component Declaration
component ClockDivider Port ( clk : in  STD_LOGIC;
        reset : in  STD_LOGIC;
        SlowClock,ledO : out  STD_LOGIC);
end component;
--Counter Component Declaration
component Counter Port (CLK,R,ENABLE,CLEAR: in std_logic;
        COUNTER :out std_logic_vector(3 downto 0));
end component;
--SevenSegmentDisplay Component Declaration
component SevenSegmentDisplay Port (input: in std_logic_vector (3 downto 0);
        output:out std_logic_vector(6 downto 0));
end component;

    begin
        --Component Instantiation
        Clock: ClockDivider port
map(CLK=>CLK,RESET=>RESET,SlowClock=>tmpCLK,ledO=>CLKoutput);
        Machine: FSM port
map(CLK=>tmpCLK,R=>RESET,START=>START,DONE=>DONE,ENABLE=>tmpEnable,CLEAR=>tmpCLEAR);
        COUNT : COUNTER port
map(CLK=>tmpClk,R=>RESET,ENABLE=>tmpEnable,CLEAR=>tmpCLEAR,COUNTER=>tmpDisplay);
        SevSeg: SevenSegmentDisplay port map(input=>tmpDisplay,output=>DISPLAY);

end Behavioral;
```

CONSTRAINTS

```
set_property IOSTANDARD LVCMOS33 [get_ports {DISPLAY[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {DISPLAY[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {DISPLAY[2]}]
```

```
set_property IOSTANDARD LVCMOS33 [get_ports {DISPLAY[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {DISPLAY[4]}]
set_property IOSTANDARD LVCMOS33 [get_ports {DISPLAY[5]}]
set_property IOSTANDARD LVCMOS33 [get_ports {DISPLAY[6]}]
set_property IOSTANDARD LVCMOS33 [get_ports CLK]
set_property IOSTANDARD LVCMOS33 [get_ports CLKoutput]
set_property IOSTANDARD LVCMOS33 [get_ports DONE]
set_property IOSTANDARD LVCMOS33 [get_ports RESET]
set_property IOSTANDARD LVCMOS33 [get_ports START]
set_property PACKAGE_PIN U7 [get_ports {DISPLAY[6]}]
set_property PACKAGE_PIN V5 [get_ports {DISPLAY[5]}]
set_property PACKAGE_PIN U5 [get_ports {DISPLAY[4]}]
set_property PACKAGE_PIN V8 [get_ports {DISPLAY[3]}]
set_property PACKAGE_PIN U8 [get_ports {DISPLAY[2]}]
set_property PACKAGE_PIN W6 [get_ports {DISPLAY[1]}]
set_property PACKAGE_PIN W7 [get_ports {DISPLAY[0]}]
set_property PACKAGE_PIN W5 [get_ports CLK]
set_property PACKAGE_PIN L1 [get_ports DONE]
set_property PACKAGE_PIN T1 [get_ports RESET]
set_property PACKAGE_PIN R2 [get_ports START]
set_property PACKAGE_PIN V3 [get_ports CLKoutput]
```