

ECEN 429: Introduction to Digital Systems Design Laboratory

North Carolina Agricultural and Technical State University

Department of Electrical and Computer Engineering

Ian Parker (Reporter)

Tayanna Lee (Lab Partner)

February, 28, 2019

Lab #5

## Introduction:


For lab 5, our focus turned to latches and flip flops. Beginning with J-K Flip Flops, which are the most versatile. Followed by D Flip Flops, which are used to store value from the data line. And finally, back to J-K Flip Flops-enhancing its functions allowing it to reset and transition from enable to disable.

**Part 1: Create a J-K Flip Flop** and demonstrate it using 7-Segment Display as an output.

Truth Table

J	K	Selector	Q	QNOT	7-Seg Display
0	0	0	Q	QNOT	QNOT
0	0	1	Q	QNOT	Q
0	1	0	0	1	1
0	1	1	0	1	0
1	0	0	1	0	0
1	0	1	1	0	1
1	1	0	Q	QNOT	Q
1	1	1	Q	QNOT	QNOT

## Schematic

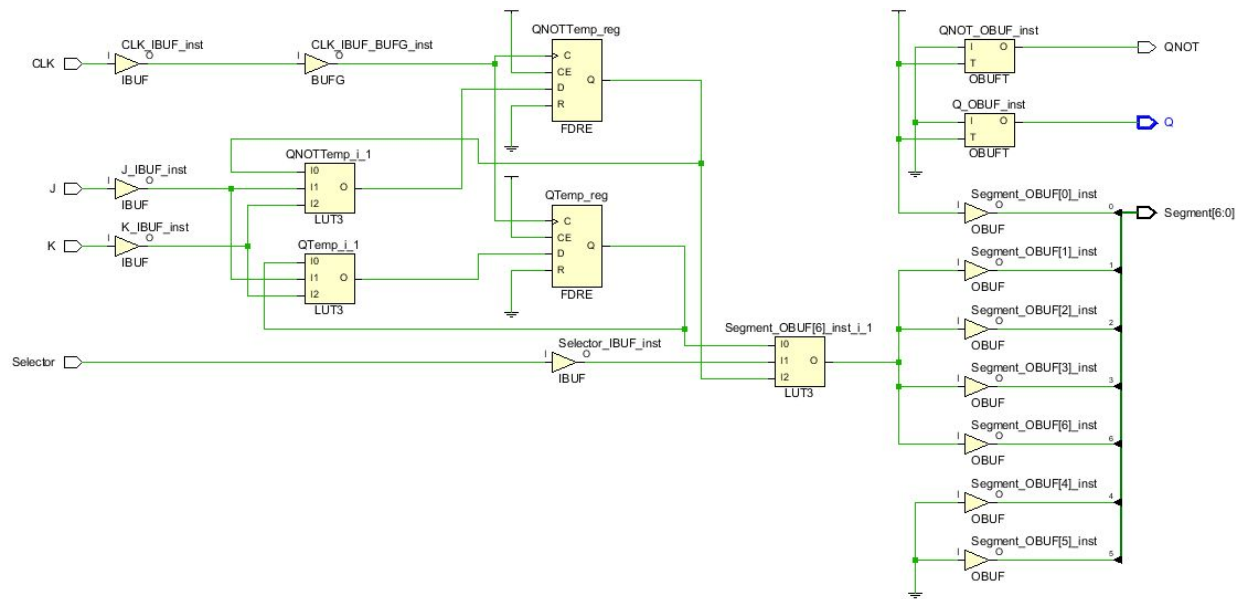

## Pin Assignment

Segment	
6	U7
5	W6
4	U8
3	V8
2	U5
1	V5
0	W7

INPUTS	
CLK	W5
J	R2

K	T1
SELECTOR	U1

## Result

 


Figure 1.1) J = 0, K=1, Selector = 0, Segment Display = 1



 



Figure 1.2) J = 1, K = 0, Selector = 0, Segment Display = 0

## Part 2: Create a D Flip-Flop Using S-R Latch and Inverter as Components

### Truth Table

D	CLK	Q	QNOT	7-Seg Display	STATE
?	0	Q	QNOT	QNOT	HOLD
0	1	0	1	0	RESET
1	1	1	0	1	SET

# Schematic

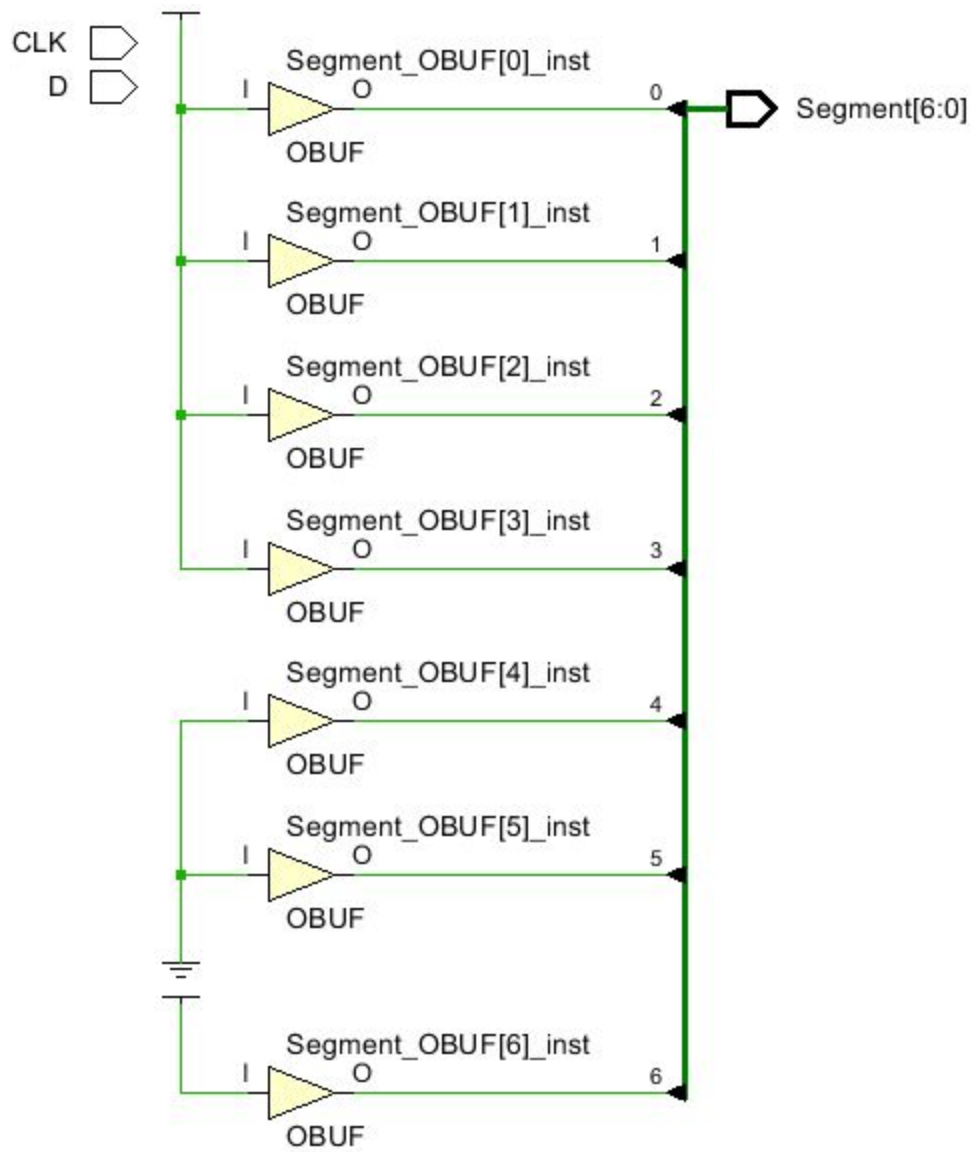

## Pin Assignment

Segment	
6	U7
5	W6
4	U8
3	V8
2	U5
1	V5
0	W7

INPUTS	
CLK	W5
D	R2

Result

 



Figure 2.1)  $D = 1$ ,  $CLK = 1$ .



**Part 3: J-K Flip Flop with a Enable and Reset feature added to it**  
**Truth Table**

J	K	ENABLE	RESET		Selector 1	Selector 0
DC	DC	DC	1		0	1
DC	DC	0	0		Q	QNOT
0	0	1	0		Q	QNOT
0	1	1	0		0	1
1	0	1	0		1	0
1	1	1	0		TOGGLE	

**Schematic**

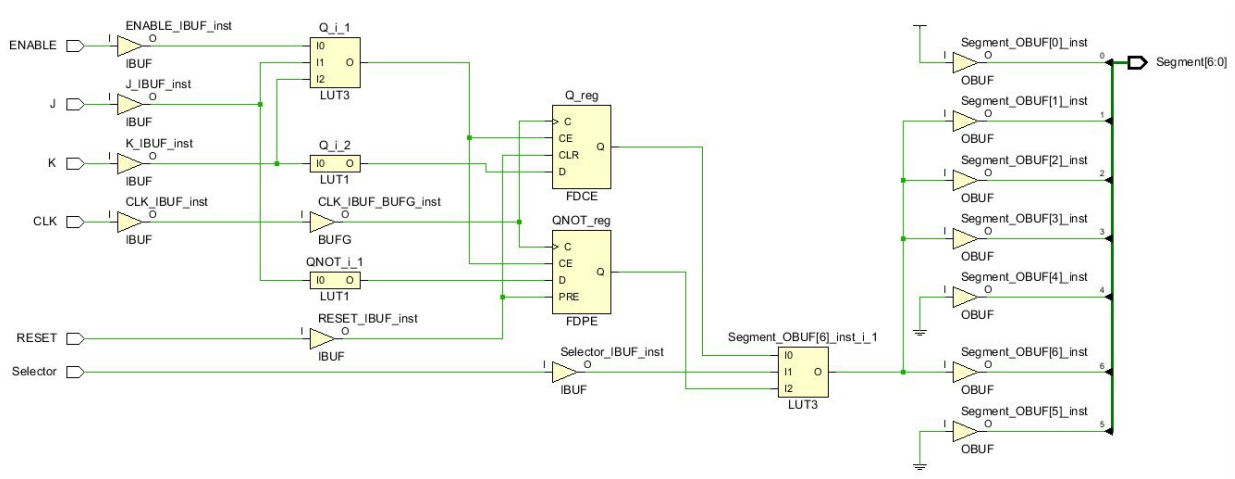

**Pin Assignment**

Segment Output	PIN
6	U7
5	W6
4	U8

3	V8
2	U5
1	V5
0	W7

<b>INPUTS</b>	<b>PIN</b>
CLK	W5
J	R2
K	T1
ENABLE	W13
RESET	W14
SELECTOR	V17

Result

 


Figure 3.1)  $J = 1$ ,  $K = 0$ ,  $ENABLE = 1$ ,  $RESET = 0$ ,  $Selector = 0$ : Thus Segment Output = 0

 


Figure 3.1) J = 1, K = 0, ENABLE = 1, RESET = 0, Selector = 1: Thus Segment Output = 1

### Conclusion:

To conclude, we became a little comfortable with coding J-K Flip Flops and D Flip Flops in VHDL. We were able to practice making particular modifications to the flip flops and how those changes made a significant difference to the truth table or how the FF moves from state to state.

### Appendices:

#### Part 1 VHDL CODE : JK FLIP FLOP

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
```



```

use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity Lab5Part1_JKFlipFlop_SourceFile is
    Port ( J,K,CLK,Selector : in STD_LOGIC;
          Q,QNOT : out STD_LOGIC;
          Segment : out STD_LOGIC_VECTOR(6 downto 0));
end Lab5Part1_JKFlipFlop_SourceFile;

architecture Behavioral of Lab5Part1_JKFlipFlop_SourceFile is
    signal QTemp, QNOTTemp, OutputTemp : STD_LOGIC;

    component TwotoOneMUX --2:1 MUX
        port (A,B,S0 : in STD_LOGIC;
              Z: out STD_LOGIC);
    end component;

    begin

        MUX : TwotoOneMUX PORT MAP (    A => QTemp,
                                         B => QNOTTemp,
                                         S0 => Selector,
                                         Z => OutputTemp);

        process(CLK)
        begin
            if(rising_edge(CLK)) then --(clk'event and (clk = '1'))
                if((J = '0') AND (K = '0')) then
                    --HOLD
                    QTemp <= QTemp;
                    QNOTTemp <= QNOTTemp;
                elsif((J = '0') AND (K = '1')) then
                    QTemp <= '0';
                    QNOTTemp <= '1';
                elsif((J = '1') AND (K = '0')) then
                    QTemp <= '1';
                    QNOTTemp <= '0';
                else
                    QTemp <= NOT J;
                    QNOTTemp <= NOT K;
                end if;
            end if;
        end process;
    end architecture;

```



```

        end if;
    end if;
end process;

process(OutputTemp)
begin
    if(OutputTemp = '0') then
        Segment <= "0000001";
    elsif(OutputTemp = '1') then
        Segment <= "1001111";
    end if;
end process;
end Behavioral;

```

## Part 1 Constraints

```

set_property IOSTANDARD LVCMOS33 [get_ports {Segment[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Segment[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Segment[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Segment[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Segment[4]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Segment[5]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Segment[6]}]
set_property IOSTANDARD LVCMOS33 [get_ports CLK]
set_property IOSTANDARD LVCMOS33 [get_ports J]
set_property IOSTANDARD LVCMOS33 [get_ports K]
set_property IOSTANDARD LVCMOS33 [get_ports Q]
set_property IOSTANDARD LVCMOS33 [get_ports QNOT]
set_property IOSTANDARD LVCMOS33 [get_ports Selector]
set_property PACKAGE_PIN R2 [get_ports J]
set_property PACKAGE_PIN U1 [get_ports Selector]
set_property PACKAGE_PIN T1 [get_ports K]
set_property PACKAGE_PIN W5 [get_ports CLK]
set_property PACKAGE_PIN V8 [get_ports {Segment[3]}]
set_property PACKAGE_PIN W7 [get_ports {Segment[0]}]
set_property PACKAGE_PIN V5 [get_ports {Segment[1]}]
set_property PACKAGE_PIN U5 [get_ports {Segment[2]}]

```

```
set_property PACKAGE_PIN U8 [get_ports {Segment[4]}]
set_property PACKAGE_PIN W6 [get_ports {Segment[5]}]
set_property PACKAGE_PIN U7 [get_ports {Segment[6]}]
```

```
set_property PACKAGE_PIN E19 [get_ports Q]
set_property PACKAGE_PIN U16 [get_ports QNOT]
```

## Part 2 VHDL Code: D-Flip Flop

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity DFlipFlop is
    Port ( D, CLK : in STD_LOGIC;
          Segment : out STD_LOGIC_VECTOR(6 downto 0));
end DFlipFlop;
```

```
architecture Behavioral of DFlipFlop is
```

```
    component SRLatch is
        port(S,R, CLK : in STD_LOGIC;
             Q, QNOT: out STD_LOGIC);
    end component;
```

```
    component INVERTER is
        port(Input : in STD_LOGIC;
             Output : out STD_LOGIC);
    end component;
```

```
    signal DTemp, DNOTTemp : STD_LOGIC;--D DNOT for the D FLip FLop
    signal SRQTemp, SRQNOTTemp : STD_LOGIC; --The Q and QNOT output for the SR
    Latch
    signal OutputTemp : STD_LOGIC;--Output
    begin
        LATCH: SRLATCH PORT MAP( D, DNOTTemp, CLK, SRQTemp, SRQNOTTemp);
        INVERT : INVERTER PORT MAP(D, DNOTTemp);
```

```

process(CLK)
begin
    if(rising_edge(CLK)) then
        if (SRQTemp = '1') then
            Segment <= "1001111";
        elsif(SRQNOTTemp = '0') then
            Segment <= "0000001";
        end if;
    end if;

end process;
end Behavioral;

```

### Part 3 VHDL Code JK Flip Flop with Reset and Enable

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity Lab5Part1_JKFlipFlop_SourceFile is
    Port ( J,K,CLK,Selector : in STD_LOGIC;
          Q,QNOT : out STD_LOGIC;
          Segment : out STD_LOGIC_VECTOR(6 downto 0));
end Lab5Part1_JKFlipFlop_SourceFile;

architecture Behavioral of Lab5Part1_JKFlipFlop_SourceFile is
    signal QTemp, QNOTTemp, OutputTemp : STD_LOGIC;

    component TwotoOneMUX --2:1 MUX
        port (A,B,S0 : in STD_LOGIC;
              Z: out STD_LOGIC);
    end component;

begin

```

```

MUX : TwotoOneMUX PORT MAP (  A => QTemp,
                               B => QNOTTemp,
                               S0 => Selector,
                               Z => OutputTemp);

process(CLK)
begin
    if(rising_edge(CLK)) then --(clk'event and (clk = '1'))
        if((J = '0') AND (K = '0')) then
            --HOLD
            QTemp <= QTemp;
            QNOTTemp <= QNOTTemp;
        elsif((J = '0') AND (K = '1')) then
            QTemp <= '0';
            QNOTTemp <= '1';
        elsif((J = '1') AND (K = '0')) then
            QTemp <= '1';
            QNOTTemp <= '0';
        else
            QTemp <= NOT J;
            QNOTTemp <= NOT K;
        end if;
    end if;
end process;

process(OutputTemp)
begin
    if(OutputTemp = '0') then
        Segment <= "0000001";
    elsif(OutputTemp = '1') then
        Segment <= "1001111";
    end if;
end process;
end Behavioral;

```

### Part 3 Constraints)

[set\\_property IOSTANDARD LVCMOS33 \[get\\_ports {Segment\[0\]}\]](#)

```
set_property IOSTANDARD LVCMOS33 [get_ports {Segment[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Segment[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Segment[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Segment[4]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Segment[5]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Segment[6]}]
set_property IOSTANDARD LVCMOS33 [get_ports CLK]
set_property IOSTANDARD LVCMOS33 [get_ports J]
set_property IOSTANDARD LVCMOS33 [get_ports K]
set_property IOSTANDARD LVCMOS33 [get_ports Q]
set_property IOSTANDARD LVCMOS33 [get_ports QNOT]
set_property IOSTANDARD LVCMOS33 [get_ports Selector]
set_property PACKAGE_PIN R2 [get_ports J]
set_property PACKAGE_PIN U1 [get_ports Selector]
set_property PACKAGE_PIN T1 [get_ports K]
set_property PACKAGE_PIN W5 [get_ports CLK]
set_property PACKAGE_PIN V8 [get_ports {Segment[3]}]
set_property PACKAGE_PIN W7 [get_ports {Segment[0]}]
set_property PACKAGE_PIN V5 [get_ports {Segment[1]}]
set_property PACKAGE_PIN U5 [get_ports {Segment[2]}]
set_property PACKAGE_PIN U8 [get_ports {Segment[4]}]
set_property PACKAGE_PIN W6 [get_ports {Segment[5]}]
set_property PACKAGE_PIN U7 [get_ports {Segment[6]}]
```

```
set_property PACKAGE_PIN E19 [get_ports Q]
set_property PACKAGE_PIN U16 [get_ports QNOT]
```