

ECEN 429: Introduction to Digital Systems Design Laboratory
North Carolina Agricultural and Technical State University
Department of Electrical and Computer Engineering

Ian Parker (Reporter)

Tayanna Lee (Lab Partner)

May 7, 2019


Lab #11

Introduction: In Lab 11 we continue to cover Vending Machines. The Vending Machine we will design will dispense either gum (0.15) or candy (0.25). It will also give the user a option to refund all the money they have entered. The Vending Machine will accept nickels(0.05) and dimes(0.10). In Lab 11 we build upon Lab 10 further by adding a countdown timer that keeps the money that the user has entered after a 5 seconds. On the FPGA board there will be a number of leds as well as a seven segment display to give a visual representation of the amount of money that has been inserted by the user, the number of gum or candy that has been added, or whether the user has enough funds.

Background: Vending Machines are found in everyday life, from schools, office buildings, or any place where people need a quick snack. In this lab we will be using a Finite State Machine design a Vending Machine which will simulate a real-life one.


Demo: <https://youtu.be/e9JhHbQQZsiA>

State Diagram

 





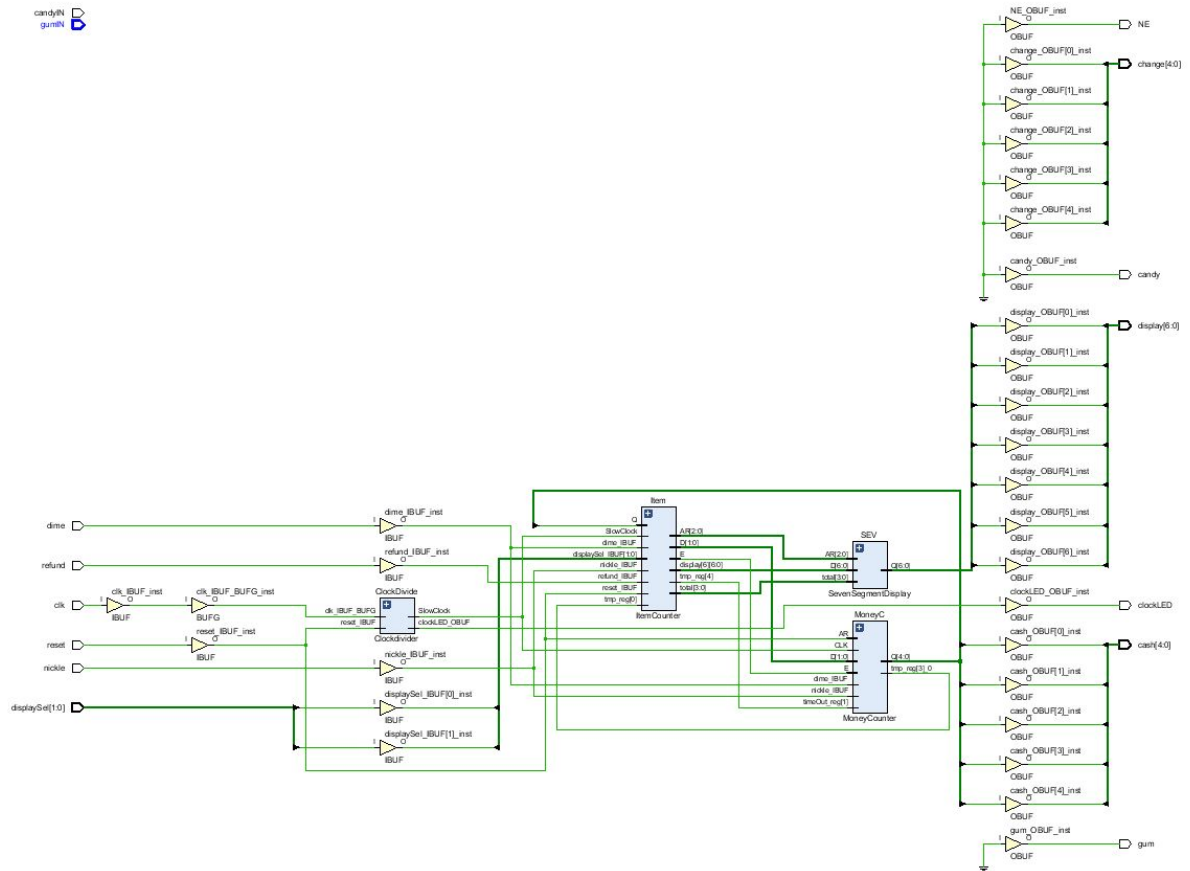

























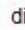

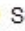



* if $time(t)=5$ go back to state 0

Schematic



PIN ASSIGNMENT

▼  All ports (30)						
▼  cash (5)	OUT		<input checked="" type="checkbox"/>	(Multiple)	LVC MOS33*	▼
 cash[4]	OUT	L1	▼ <input checked="" type="checkbox"/>	35	LVC MOS33*	▼
 cash[3]	OUT	P1	▼ <input checked="" type="checkbox"/>	35	LVC MOS33*	▼
 cash[2]	OUT	N3	▼ <input checked="" type="checkbox"/>	35	LVC MOS33*	▼
 cash[1]	OUT	P3	▼ <input checked="" type="checkbox"/>	35	LVC MOS33*	▼
 cash[0]	OUT	U3	▼ <input checked="" type="checkbox"/>	34	LVC MOS33*	▼
▼  change (5)	OUT		<input checked="" type="checkbox"/>	14	LVC MOS33*	▼
 change[4]	OUT	W18	▼ <input checked="" type="checkbox"/>	14	LVC MOS33*	▼
 change[3]	OUT	V19	▼ <input checked="" type="checkbox"/>	14	LVC MOS33*	▼
 change[2]	OUT	U19	▼ <input checked="" type="checkbox"/>	14	LVC MOS33*	▼
 change[1]	OUT	E19	▼ <input checked="" type="checkbox"/>	14	LVC MOS33*	▼
 change[0]	OUT	U16	▼ <input checked="" type="checkbox"/>	14	LVC MOS33*	▼
▼  display (7)	OUT		<input checked="" type="checkbox"/>	34	LVC MOS33*	▼
 display[6]	OUT	W7	▼ <input checked="" type="checkbox"/>	34	LVC MOS33*	▼
 display[5]	OUT	W6	▼ <input checked="" type="checkbox"/>	34	LVC MOS33*	▼
 display[4]	OUT	U8	▼ <input checked="" type="checkbox"/>	34	LVC MOS33*	▼
 display[3]	OUT	V8	▼ <input checked="" type="checkbox"/>	34	LVC MOS33*	▼
 display[2]	OUT	U5	▼ <input checked="" type="checkbox"/>	34	LVC MOS33*	▼
 display[1]	OUT	V5	▼ <input checked="" type="checkbox"/>	34	LVC MOS33*	▼
 display[0]	OUT	U7	▼ <input checked="" type="checkbox"/>	34	LVC MOS33*	▼
▼  displaySel (2)	IN		<input checked="" type="checkbox"/>	14	LVC MOS33*	▼
 displaySel[1]	IN	V16	▼ <input checked="" type="checkbox"/>	14	LVC MOS33*	▼
 displaySel[0]	IN	V17	▼ <input checked="" type="checkbox"/>	14	LVC MOS33*	▼
▼  Scalar ports (11)						
 candy	OUT	V14	▼ <input checked="" type="checkbox"/>	14	LVC MOS33*	▼
 candyIN	IN	R2	▼ <input checked="" type="checkbox"/>	34	LVC MOS33*	▼
 clk	IN	W5	▼ <input checked="" type="checkbox"/>	34	LVC MOS33*	▼
 clockLED	OUT	V13	▼ <input checked="" type="checkbox"/>	14	LVC MOS33*	▼
 dime	IN	R3	▼ <input checked="" type="checkbox"/>	34	LVC MOS33*	▼
 gum	OUT	U14	▼ <input checked="" type="checkbox"/>	14	LVC MOS33*	▼
 gumIN	IN	T1	▼ <input checked="" type="checkbox"/>	34	LVC MOS33*	▼
 NE	OUT	W3	▼ <input checked="" type="checkbox"/>	34	LVC MOS33*	▼
 nickle	IN	W2	▼ <input checked="" type="checkbox"/>	34	LVC MOS33*	▼
 refund	IN	T2	▼ <input checked="" type="checkbox"/>	34	LVC MOS33*	▼
 reset	IN	U1	▼ <input checked="" type="checkbox"/>	34	LVC MOS33*	▼

Results

 


Figure 1.1) System initial state, no money has been added. Nothing selected

 


Figure 1.2) System initial state, no money has been added. Candy Selected, shows not enough money for candy

 


Figure 1.3) dime has been added

Conclusion: This lab gave us more hands on experience with FPGA boards and helped us to understand more complex logic systems including a timer. The amount decisions that can be made in each state at first seemed to be complex but as we progressed through the design it became much more clear. This lab put to the test our understanding of everything that we have designed before this, building on top of our understanding of finite state machines. A fitting final lab.

Appendices

VHDL

SevenSegmentDisplay

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity SevenSegmentDisplay is
    Port (ip : in std_logic_vector(3 downto 0);
          display : out std_logic_vector(6 downto 0));
end SevenSegmentDisplay;

architecture Behavioral of SevenSegmentDisplay is

begin
    process(ip)
    begin
        if(ip = "0000") then display <= "0000001";--0
        elsif(ip = "0001") then display <= "1001111";
        elsif(ip = "0010") then display <= "0010010";
        elsif(ip = "0011") then display <= "0000110";
        elsif(ip = "0100") then display <= "1001100";
        elsif(ip = "0101") then display <= "0100100";
        elsif(ip = "0110") then display <= "0100000";
        elsif(ip = "0111") then display <= "0001111";
        elsif(ip = "1000") then display <= "0000000";
        elsif(ip = "1001") then display <= "0001100";
        elsif(ip = "1010") then display <= "0001000";
        elsif(ip = "1011") then display <= "1000110";
        elsif(ip = "1100") then display <= "0110001";
        elsif(ip = "1101") then display <= "1000110";
        elsif(ip = "1110") then display <= "0110000";
        elsif(ip = "1111") then display <= "0110000";--F
        end if;
    end process;

end Behavioral;
```

ClockDivider

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use ieee.std_logic_unsigned.all;

entity Clockdivider is
```

```

Port ( clk : in  STD_LOGIC;
      reset : in  STD_LOGIC;
      SlowClock,ledO : out STD_LOGIC);
end Clockdivider;

```

architecture behavioral of Clockdivider is

```

signal slowSig: std_logic;
begin
  process
    variable cnt :  std_logic_vector(26 downto 0):= "000000000000000000000000";
    begin
      -- calculations
      wait until ((clk'EVENT) AND (clk = '1'));
      if (reset = '1') then
        cnt := "000000000000000000000000";
      else
        cnt := cnt + 1; -- count to 26
      end if;

      SlowClock <= cnt(26);
      slowSig<=cnt(26);

      if(slowSig='1')then
        ledO<='1';
      else
        ledO<='0';
      end if;

    end process;
end Behavioral;

```

TopLevel

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

```

entity TopLevel is

```

Port (clk,reset,gumIN,candyIN,refund,nickle,dime: in std_logic;
      displaySel:in std_logic_vector(1 downto 0);--what needs to be displayed
      gum,candy:out std_logic;
      display:out std_logic_vector(6 downto 0);
      cash:out std_logic_vector(4 downto 0);
      change: out std_logic_vector(4 downto 0);
      clockLED,NE: out std_logic);
end TopLevel;

```

architecture Behavioral of TopLevel is

```

signal nickleSig,dimeSig,gumOut,candyOut,clockOut,refundtmp,tmpTime: std_logic;
signal total,outTimetmp: std_logic_vector(3 downto 0);

```



```

component countdown port (clk,reset,coin:in std_logic;
                        countTime:out std_logic_vector(3 downto 0));
end component;

component clockDivider port( clk : in STD_LOGIC;
                        reset : in STD_LOGIC;
                        SlowClock,ledO : out STD_LOGIC);
end component;

component VM port (clk,reset,gumSel,candySel,refund,nickle,dime: in std_logic;
                timeIN: in std_logic_vector(3 downto 0);
                nickleCount,dimeCount,NotEnough,gum,candy,startTime:out std_logic;
                change:out std_logic_vector(4 downto 0));
end component;

component MoneyCounter port (clk,reset,nickleIN,dimeIN,gumOut,candyOut,refund:in std_logic;
                        timeIN:in std_logic_vector(3 downto 0);
                        moneyCount:out std_logic_vector(4 downto 0));
end component;

component ItemCounter Port (clk,reset,candyIN,gumIN,startTimer:in std_logic;
                        sel : in std_logic_vector(1 downto 0);--chose which total you want to see displayed
                        timeOut: out std_logic_vector(3 downto 0);
                        total : out std_logic_vector(3 downto 0));
end component;

component SevenSegmentDisplay port ( ip : in std_logic_vector(3 downto 0);
                        display : out std_logic_vector(6 downto 0));
end component;

begin

refundtmp<=refund;
gum<=gumOut;
candy<=candyOut;

ClockDivide: ClockDivider port map(clk=>clk,
                        reset=>reset,
                        SlowClock=>clockOut,
                        ledO=>clockLED);
Machine: VM port map( clk=>clockOut,
                        reset=>reset,
                        gumSel=> gumIN,
                        candySel=>candyIN,

```

```

refund=>refundtmp,
nickle=>nickle,
dime=>dime,
timeIN=>outTimetmp,
nickleCount=>nickleSig,
dimeCount=>dimeSig,
NotEnough=>NE,
gum=>gumOut,
candy=>candyOut,
startTime=>tmpTime,
change=>change);

```

```

MoneyC: MoneyCounter port map(clk=>clockOut,
    reset=>reset,
    nickleIN=>nickleSig,
    dimeIN=>dimeSig,
    gumOut=>gumOut,
    candyOut=>candyOut,
    refund =>refundtmp,
    timeIN=>outTimetmp,
    moneyCount=>cash);

```

```

Item: ItemCounter port map(clk=>clockOut,
    reset=>reset,
    candyIN=>candyOut,
    gumIN=>gumOut,
    startTimer=>tmpTime,
    sel=>displaySel,
    timeOut=>outTimetmp,
    total=>total);

```

```

SEV:SevenSegmentDisplay port map(ip=>total,display=>display);

```

```

end Behavioral;

```

Vending Machine

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

```

```

entity VM is

```

```

    Port (clk,reset,gumSel,candySel,refund,nickle,dime: in std_logic;
        timeIN: in std_logic_vector(3 downto 0);
        nickleCount,dimeCount,NotEnough,gum,candy,startTime:out std_logic;
        change:out std_logic_vector(4 downto 0));

```

```
end VM;
```

architecture Behavioral of VM is

```
type state_type is (S0,S5,S10,S15,S20,S25,S30);
```

```
signal cs,ns: state_type;
```

```
begin
```

```
process(clk,reset)
```

```
begin
```

```
if (reset='1')then
```

```
cs<=S0;
```

```
elsif(clk'event AND clk='1')then
```

```
cs<=ns;
```

```
end if;
```

```
end process;
```

```
process(cs,nickle,dime,refund,gumSel,candySel)
```

```
begin
```

```
--initilization
```

```
startTime<='1';
```

```
NotEnough<='0';
```

```
gum<='0';
```

```
candy<='0';
```

```
change<="00000";
```

```
nickleCount<=nickle;
```

```
dimeCount<=dime;
```

```
case cs is
```

```
when S0=>
```

```
if(timeIN< "0101" and (refund='1' or gumSel='1' or candySel='1' or nickle='1' or dime='1'))then
```

```
if(refund<='1')then
```

```
change<="00000";
```

```
startTime<='0';
```

```
ns<=S0;
```

```
elsif(gumSel='1' or candySel='1')then
```

```
NotEnough<='1';
```

```
startTime<='0';
```

```
ns<=S0;
```

```
elsif(nickle='1')then
```

```
startTime<='0';
```

```
ns<=S5;
```

```
elsif(dime='1')then
```

```
startTime<='0';
```

```
ns<=S10;
```

```
end if;
```

```
elsif(timeIN>="0101" and(refund='0' or gumSel='0' or candySel='0' or nickle='0' or dime='0')) then
```

```
ns<=s0;
```

```
end if;
```

```
startTime<='1';
```

```

when S5=>
  if(timeIN< "0101" and (refund='1' or gumSel='1' or candySel='1' or nickle='1' or dime='1'))then
    if(refund<='1')then
      change<="00101";
      startTime<='0';
      ns<=S0;
    elseif(gumSel='1' or candySel='1')then
      NotEnough<='1';
      startTime<='0';
      ns<=S5;
    elseif(nickle='1')then
      startTime<='0';
      ns<=S10;
    elseif(dime='1')then
      startTime<='0';
      ns<=S15;
    end if;
  elseif(timeIN>="0101" and (refund='0' or gumSel='0' or candySel='0' or nickle='0' or dime='0')) then
    ns<=s0;
    startTime<='0';
  end if;
  startTime<='1';
when S10=>
  if(timeIN< "0101" and (refund='1' or gumSel='1' or candySel='1' or nickle='1' or dime='1'))then
    if(refund<='1')then
      change<="01010";
      startTime<='0';
      ns<=S0;
    elseif(gumSel='1' or candySel='1')then
      NotEnough<='1';
      startTime<='0';
      ns<=S10;
    elseif(nickle='1')then
      startTime<='0';
      ns<=S15;
    elseif(dime='1')then
      startTime<='0';
      ns<=S20;
    end if;
  elseif(timeIN>="0101" and (refund='0' or gumSel='0' or candySel='0' or nickle='0' or dime='0')) then
    ns<=s0;
    startTime<='0';
  end if;
  startTime<='1';
when S15=>
  if(timeIN< "0101" and (refund='1' or gumSel='1' or candySel='1' or nickle='1' or dime='1'))then
    if(refund<='1')then
      change<="01111";

```



```

        startTime<='0';
        ns<=S0;
    elseif(candySel='1')then
        NotEnough<='1';
        startTime<='0';
        ns<=S15;
    elseif(gumSel='1')then
        gum<='1';
        startTime<='0';
        ns<=S0;
    elseif(nickle='1')then
        startTime<='0';
        ns<=S20;
    elseif(dime='1')then
        startTime<='0';
        ns<=S25;
    end if;
elseif(timeIN>="0101" and(refund='0' or gumSel='0' or candySel='0' or nickle='0' or dime='0')) then
    ns<=s0;
    startTime<='0';
end if;
    startTime<='1';
when S20=>
    if(timeIN< "0101" and (refund='1' or gumSel='1' or candySel='1' or nickle='1' or dime='1'))then
        if(refund<='1')then
            change<="10100";
            startTime<='0';
            ns<=S0;
        elseif(candySel='1')then
            NotEnough<='1';
            startTime<='0';
            ns<=S20;
        elseif(gumSel='1')then
            gum<='1';
            startTime<='0';
            ns<=S0;
            change<="00101";
        elseif(nickle='1')then
            startTime<='0';
            ns<=S25;
        elseif(dime='1')then
            startTime<='0';
            ns<=S30;
        end if;
    elseif(timeIN>="0101" and(refund='0' or gumSel='0' or candySel='0' or nickle='0' or dime='0')) then
        ns<=s0;
        startTime<='0';
    end if;

```

```

    startTime<='1';
when S25=>
    if(timeIN< "0101" and (refund='1' or gumSel='1' or candySel='1' or nickle='1' or dime='1'))then
        if(refund<='1')then
            change<="11001";
            startTime<='0';
            ns<=S0;
        elsif(candySel='1')then
            candy<='1';
            startTime<='0';
            ns<=S0;
        elsif(gumSel='1')then
            change<="01010";
            gum<='1';
            startTime<='0';
            ns<=S0;
        elsif(nickle='1')then
            startTime<='0';
            ns<=S30;
        elsif(dime='1')then
            startTime<='0';
            ns<=S30;
        end if;
    elsif(timeIN>="0101" and (refund='0' or gumSel='0' or candySel='0' or nickle='0' or dime='0')) then
        ns<=s0;
        startTime<='0';
    end if;
    startTime<='1';
when S30=>
    if(timeIN< "0101" and (refund='1' or gumSel='1' or candySel='1' or nickle='1' or dime='1'))then
        if(refund<='1')then
            change<="11110";
            startTime<='0';
            ns<=S0;
        elsif(candySel='1')then
            change<="00101";
            candy<='1';
            startTime<='0';
            ns<=S0;
        elsif(gumSel='1')then
            change<="01111";
            gum<='1';
            startTime<='0';
            ns<=S0;
        elsif(nickle='1')then
            startTime<='0';
            ns<=S30;
            change<="00101";
        end if;
    end if;
end when;

```

```

        elsif(dime='1')then
            startTime<='0';
            ns<=S30;
            change<="01010";
        end if;
    elsif(timeIN>="0101" and(refund='0' or gumSel='0' or candySel='0' or nickle='0' or dime='0')) then
        ns<=s0;
        startTime<='0';
    end if;
    startTime<='1';
end case;
end process;
end Behavioral;

```

Item Counter

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity ItemCounter is
    Port (clk,reset,candyIN,gumIN,startTimer:in std_logic;
        sel : in std_logic_vector(1 downto 0);--chose which total you want to see displayed
        timeOut: out std_logic_vector(3 downto 0);
        total : out std_logic_vector(3 downto 0));
end ItemCounter;

architecture Behavioral of ItemCounter is
    signal tmpG,tmpC,tmpTime :std_logic_vector(3 downto 0);--gum and candy
begin

    process(clk,reset)
    begin
        if(reset='1')then
            tmpG<="0000";
            tmpC<="0000";
            tmpTime<="0000";
        elsif(clk'event and clk='1')then
            if(gumIN='1')then
                tmpG<=tmpG + "0001"; --increment
            end if;
            if(candyIN='1')then
                tmpC<=tmpC + "0001"; --increment
            end if;

            --for the timer
            if(startTimer='1')then
                if(tmpTime<"0101")then

```

```

        tmpTime<=tmpTime + "0001"; --increments timer
        timeOut<=tmpTime;
    end if;
    if(tmpTime>="0101")then
        tmpTime<="0000";
        timeOut<=tmpTime;
    end if;
end if;
--if the timer aint start
if(startTimer='0')then
    tmpTime<="0000";
end if;

--based on selector...
if(sel="00")then
    total<=tmpG;--displau the total gum
elsif(sel="01")then
    total<=tmpC;--display the total candy
elsif(sel="01")then
    total<=tmpTime;--display the total candy
end if;
end if;
end process;
end Behavioral;

```

Money Counter

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity MoneyCounter is
    Port (clk,reset,nickleIN,dimeIN,gumOut,candyOut,refund:in std_logic;
        timeIN:in std_logic_vector(3 downto 0);
        moneyCount:out std_logic_vector(4 downto 0));
end MoneyCounter;

architecture Behavioral of MoneyCounter is
    signal tmp: std_logic_vector(4 downto 0);--amount of money insterted
begin
    process(clk,reset)
    begin
        if (reset='1')then
            tmp<="00000";--restock
        elsif(clk'event and clk='1')then
            if(nickleIN='1')then--if nickle is inserted
                tmp<=tmp + "0101"; --add nickel(5 cents)
            elsif(dimeIN='1')then--if dime is inserted

```



```

        tmp<=tmp + "1010";--add dime(10 cents)
    elsif(gumOut='1' or candyOut='1')then--if gum or candy is selected
        tmp<="00000";--revert to no money entered
    elsif(refund='1')then--refund is high
        tmp<="00000";
    end if;

    if(timeIN="0101")then
        tmp<="00000";
    end if;
end if;

    moneyCount<=tmp;
end process;
end Behavioral;

```

Countdown

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity countdown is
    Port (clk,reset,coin:in std_logic;
        countTime:out std_logic_vector(3 downto 0));
end countdown;

architecture Behavioral of countdown is
    signal tmp: std_logic_vector(3 downto 0);
begin

    tmp<="0000"; --setting these to 15 so the counter can show how many are left in machine
    process(clk,reset)
    begin
        if (reset='1')then
            tmp<="0000";
        elsif(clk'event and clk='1')then
            if(coin='1')then
                if(tmp<"0101")then
                    tmp<=tmp + "0001"; --increments countdown
                end if;
            end if;
        end if;
        countTime<=tmp;
    end process;

end Behavioral;

```

Constraints

```
set_property IOSTANDARD LVCMOS33 [get_ports {change[4]}]
set_property IOSTANDARD LVCMOS33 [get_ports {change[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {change[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {change[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {change[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {display[6]}]
set_property IOSTANDARD LVCMOS33 [get_ports {display[5]}]
set_property IOSTANDARD LVCMOS33 [get_ports {display[4]}]
set_property IOSTANDARD LVCMOS33 [get_ports {display[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {display[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {display[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {display[0]}]
set_property PACKAGE_PIN W18 [get_ports {change[4]}]
set_property PACKAGE_PIN V19 [get_ports {change[3]}]
set_property PACKAGE_PIN U19 [get_ports {change[2]}]
set_property PACKAGE_PIN E19 [get_ports {change[1]}]
set_property PACKAGE_PIN U16 [get_ports {change[0]}]
set_property PACKAGE_PIN W7 [get_ports {display[6]}]
set_property PACKAGE_PIN W6 [get_ports {display[5]}]
set_property PACKAGE_PIN U8 [get_ports {display[4]}]
set_property PACKAGE_PIN V8 [get_ports {display[3]}]
set_property PACKAGE_PIN U5 [get_ports {display[2]}]
set_property PACKAGE_PIN V5 [get_ports {display[1]}]
set_property PACKAGE_PIN U7 [get_ports {display[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports clockLED]
set_property IOSTANDARD LVCMOS33 [get_ports dime]
set_property IOSTANDARD LVCMOS33 [get_ports refund]
set_property IOSTANDARD LVCMOS33 [get_ports reset]
set_property PACKAGE_PIN V13 [get_ports clockLED]
set_property PACKAGE_PIN R3 [get_ports dime]
set_property PACKAGE_PIN T2 [get_ports refund]
set_property PACKAGE_PIN U1 [get_ports reset]
```

```
set_property PACKAGE_PIN W5 [get_ports clk]
set_property IOSTANDARD LVCMOS33 [get_ports clk]
```

```
set_property PACKAGE_PIN V14 [get_ports candy]
set_property IOSTANDARD LVCMOS33 [get_ports candy]
set_property IOSTANDARD LVCMOS33 [get_ports {displaySel[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {displaySel[1]}]
set_property PACKAGE_PIN U14 [get_ports gum]
set_property PACKAGE_PIN W3 [get_ports NE]
set_property PACKAGE_PIN W2 [get_ports nickle]
set_property IOSTANDARD LVCMOS33 [get_ports gum]
```

```
set_property IOSTANDARD LVCMOS33 [get_ports NE]
set_property IOSTANDARD LVCMOS33 [get_ports nickle]
```

```
set_property IOSTANDARD LVCMOS33 [get_ports {cash[4]}]
set_property IOSTANDARD LVCMOS33 [get_ports {cash[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {cash[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {cash[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {cash[0]}]
set_property PACKAGE_PIN N3 [get_ports {cash[2]}]
set_property PACKAGE_PIN L1 [get_ports {cash[4]}]
set_property PACKAGE_PIN P3 [get_ports {cash[1]}]
set_property PACKAGE_PIN P1 [get_ports {cash[3]}]
set_property PACKAGE_PIN U3 [get_ports {cash[0]}]
```

```
set_property PACKAGE_PIN V17 [get_ports {displaySel[0]}]
set_property PACKAGE_PIN V16 [get_ports {displaySel[1]}]
```

```
set_property IOSTANDARD LVCMOS33 [get_ports candyIN]
set_property IOSTANDARD LVCMOS33 [get_ports gumIN]
set_property PACKAGE_PIN R2 [get_ports candyIN]
set_property PACKAGE_PIN T1 [get_ports gumIN]
```