

ECEN 429: Introduction to Digital Systems Design Laboratory

North Carolina Agricultural and Technical State University

Department of Electrical and Computer Engineering

Ian Parker (Reporter)

Tayanna Lee (Lab Partner)

March 28, 2019

Lab #7

Introduction:

For lab 7, we had to create an ALU with four different functions and a FSM. We then took these two separate programs and produced components from both, in order to develop a top-level design that performs a different function based upon the current state. We also implemented the seven segment display to show the results of those functions being executed.

Part 1: ALU

TRUTH TABLE


For two inputs A and B

SELECT(CASE)	OUTPUT (OPERATION)
00	XOR
01	NAND
10	ADD
11	SUBTRACT

PIN ASSIGNMENTS

All ports (17)									
Ao (4)		IN					<input checked="" type="checkbox"/>	14	LVC MOS33*
	Ao[3]	IN			W17		<input checked="" type="checkbox"/>	14	LVC MOS33*
	Ao[2]	IN			W16		<input checked="" type="checkbox"/>	14	LVC MOS33*
	Ao[1]	IN			V16		<input checked="" type="checkbox"/>	14	LVC MOS33*
	Ao[0]	IN			V17		<input checked="" type="checkbox"/>	14	LVC MOS33*
Bo (4)		IN					<input checked="" type="checkbox"/>	34	LVC MOS33*
	Bo[3]	IN			R2		<input checked="" type="checkbox"/>	34	LVC MOS33*
	Bo[2]	IN			T1		<input checked="" type="checkbox"/>	34	LVC MOS33*
	Bo[1]	IN			U1		<input checked="" type="checkbox"/>	34	LVC MOS33*
	Bo[0]	IN			W2		<input checked="" type="checkbox"/>	34	LVC MOS33*
OUTPUTo (7)		OUT					<input checked="" type="checkbox"/>	34	LVC MOS33*
	OUTPUTo[6]	OUT			U7		<input checked="" type="checkbox"/>	34	LVC MOS33*
	OUTPUTo[5]	OUT			V5		<input checked="" type="checkbox"/>	34	LVC MOS33*
	OUTPUTo[4]	OUT			U5		<input checked="" type="checkbox"/>	34	LVC MOS33*
	OUTPUTo[3]	OUT			V8		<input checked="" type="checkbox"/>	34	LVC MOS33*
	OUTPUTo[2]	OUT			U8		<input checked="" type="checkbox"/>	34	LVC MOS33*
	OUTPUTo[1]	OUT			W6		<input checked="" type="checkbox"/>	34	LVC MOS33*
	OUTPUTo[0]	OUT			W7		<input checked="" type="checkbox"/>	34	LVC MOS33*
SELo (2)		IN					<input checked="" type="checkbox"/>	14	LVC MOS33*
	SELo[1]	IN			W13		<input checked="" type="checkbox"/>	14	LVC MOS33*
	SELo[0]	IN			W14		<input checked="" type="checkbox"/>	14	LVC MOS33*

SCHEMATIC

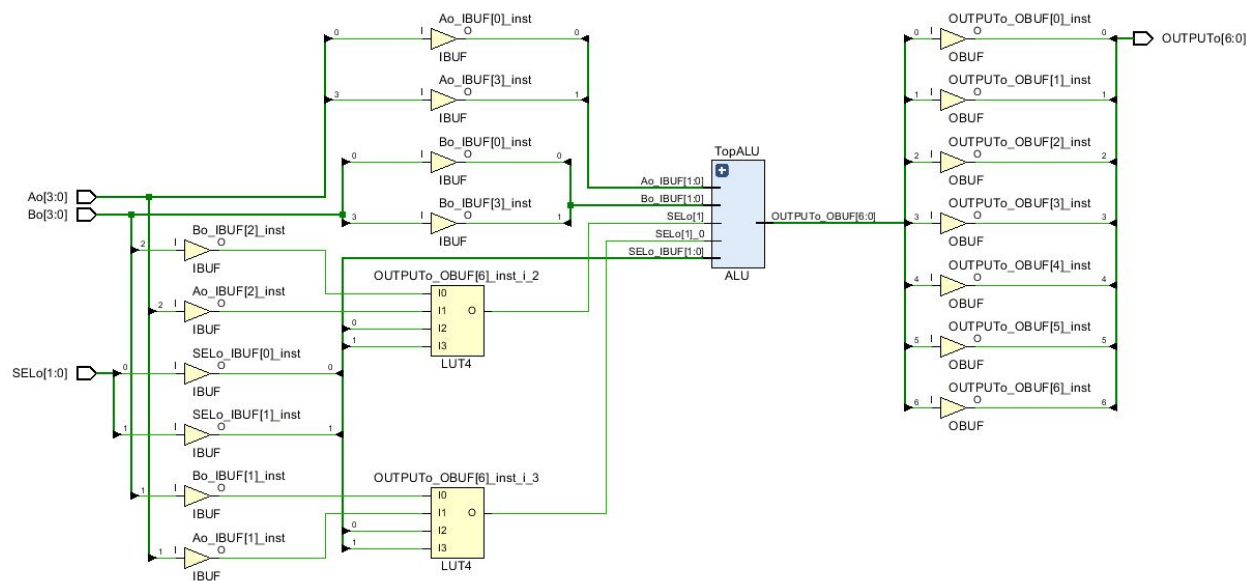

RESULT

 


Figure 1.1) $B(0000) \text{ XOR } A(0001) = (0001)$ or 1 in HEX


 


Figure 1.2) $B(0000) \text{ NAND } A(0001) = (1111)$ or F in HEX

PART 2: FSM


STATE DIAGRAM

 

PIN ASSIGNMENTS

All ports (13)												
CommandLed (2)	OUT							<input checked="" type="checkbox"/>	35	LVC MOS33*		
CommandLed[1]	OUT					L1		<input checked="" type="checkbox"/>	35	LVC MOS33*		
CommandLed[0]	OUT					P1		<input checked="" type="checkbox"/>	35	LVC MOS33*		
OUTPUTo (7)	OUT							<input checked="" type="checkbox"/>	34	LVC MOS33*		
OUTPUTo[6]	OUT					U7		<input checked="" type="checkbox"/>	34	LVC MOS33*		
OUTPUTo[5]	OUT					V5		<input checked="" type="checkbox"/>	34	LVC MOS33*		
OUTPUTo[4]	OUT					U5		<input checked="" type="checkbox"/>	34	LVC MOS33*		
OUTPUTo[3]	OUT					V8		<input checked="" type="checkbox"/>	34	LVC MOS33*		
OUTPUTo[2]	OUT					U8		<input checked="" type="checkbox"/>	34	LVC MOS33*		
OUTPUTo[1]	OUT					W6		<input checked="" type="checkbox"/>	34	LVC MOS33*		
OUTPUTo[0]	OUT					W7		<input checked="" type="checkbox"/>	34	LVC MOS33*		
Scalar ports (4)												
CLKled	OUT					V3		<input checked="" type="checkbox"/>	34	LVC MOS33*		
CLKo	IN					W5		<input checked="" type="checkbox"/>	34	LVC MOS33*		
INPUTo	IN					R2		<input checked="" type="checkbox"/>	34	LVC MOS33*		
RESETo	IN					T1		<input checked="" type="checkbox"/>	34	LVC MOS33*		

SCHEMATIC

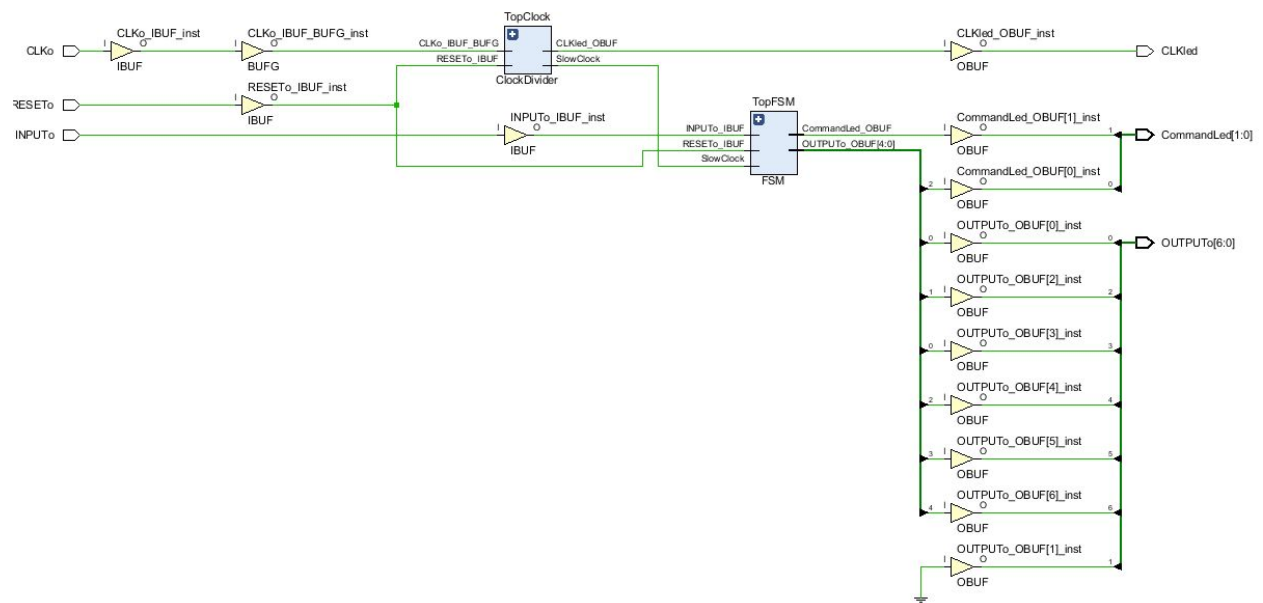

RESULTS

 


Figure 2.1) INPUT = 1 and CLOCK is high. Here we see that the Command issued is (01) and the State is (1)

 


Figure 2.2) INPUT = 1 and CLOCK is high. Here we see that the Command issued is (10) and the State is (2)


PART 3: ALU-FSM Combined

TRUTH TABLE for ALU


For two inputs A and B

SELECT(CASE)	OUTPUT (OPERATION)
00	XOR
01	NAND
10	ADD
11	SUBTRACT

STATE DIAGRAM

 

Schematic

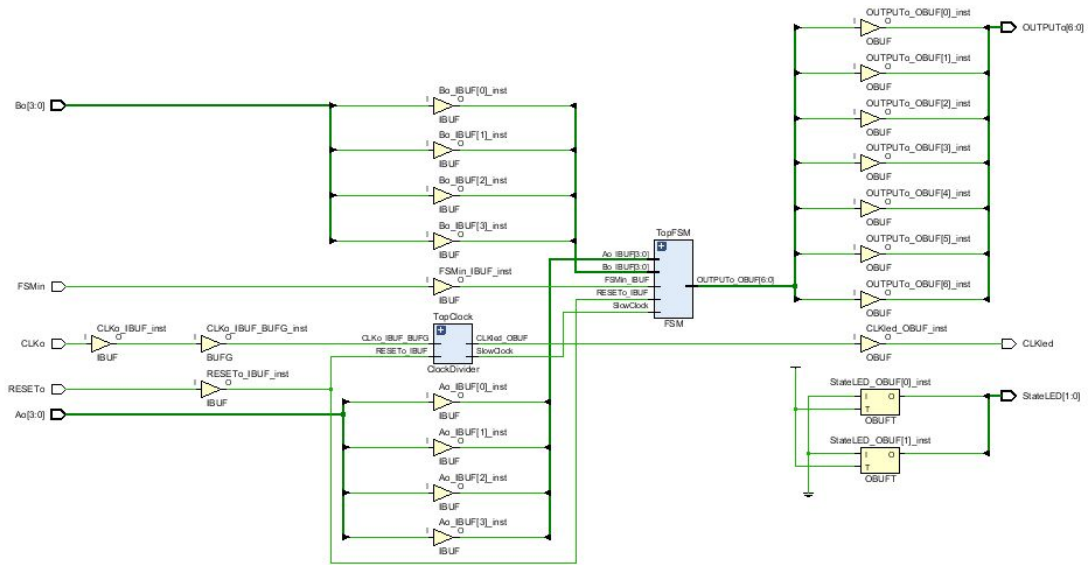

PIN ASSIGNMENTS

✎ All ports (21)

✎ Ao (4)	IN					
✎ Ao[3]	IN				W17	▼
✎ Ao[2]	IN				W16	▼
✎ Ao[1]	IN				V16	▼
✎ Ao[0]	IN				V17	▼
✎ Bo (4)	IN					
✎ Bo[3]	IN				R2	▼
✎ Bo[2]	IN				T1	▼
✎ Bo[1]	IN				U1	▼
✎ Bo[0]	IN				W2	▼
✎ OUTPUTo (7)	OUT					
✎ OUTPUTo[6]	OUT				U7	▼
✎ OUTPUTo[5]	OUT				V5	▼
✎ OUTPUTo[4]	OUT				U5	▼
✎ OUTPUTo[3]	OUT				V8	▼
✎ OUTPUTo[2]	OUT				U8	▼
✎ OUTPUTo[1]	OUT				W6	▼
✎ OUTPUTo[0]	OUT				W7	▼
✎ StateLED (2)	OUT					
✎ StateLED[1]	OUT				E19	▼
✎ StateLED[0]	OUT				U16	▼
✎ Scalar ports (4)						
✎ CLKled	OUT				V3	▼
✎ CLKo	IN				W5	▼
✎ FSMIn	IN				T3	▼
✎ RESETo	IN				V2	▼

RESULTS

 


Figure 3.1) INPUT = 1 and CLOCK is high. State(00). $B(0000) \text{ XOR } A(0001) = (0001)$ or 1 in HEX.

 


Figure 3.2) INPUT = 0 and CLOCK is high but RESET = 1 State(00). B(0000) XOR A(0000) = (0000) or 0 in HEX.

Conclusion:

In conclusion, this continues to strengthen our use of components and understanding of FSM, and how they can be used as a control unit (in this case the ALU). This very difficult lab should give us a cushion for the labs to come, when it comes to implementing FSMs.

Appendices:

PART1

ALU

```
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.std_logic_unsigned.all;  
use ieee.numeric_std.all;
```

entity ALU is

```
    port(A,B : in std_logic_vector(3 downto 0);  
          SEL : in std_logic_vector(1 downto 0);  
          OUTPUT: out std_logic_vector (3 downto 0));  
end;
```

architecture Behavioral of ALU is

signal OutTemp, XOROutTemp : std_logic_vector(3 downto 0); --holds value for output of A
 and B XORed, which will be shifted. Also a regular output temp signal

```
    begin  
    process(SEL)  
    begin  
        if(SEL = "00") then  
            OutTemp <= A XOR B; --XOR  
            XOROutTemp <= OutTemp;  
        elsif(SEL = "01") then  
            OutTemp <= A NAND B; --NAND  
        elsif(SEL = "10") then  
            OutTemp <= (A NAND B) + "0100"; --ADD 4 to the inputs Nanded  
        elsif(SEL = "11") then  
            OutTemp <= (A NAND B) - "0010"; --SUBTRACT 2 to the inputs Nanded  
        end if;  
    end process;  
    OUTPUT <= OutTemp;  
end Behavioral;
```

DISPLAY

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Display is
    port(Input :in std_logic_vector(3 downto 0);
          Output :out std_logic_vector(6 downto 0));
end Display;
```

architecture Behavioral of Display is

```
begin
    process (Input)
    begin
        case Input is
            --Individual Segments
            when "0000" => Output <= "1000000"; --0
            when "0001" => Output <= "1111001"; --1
            when "0010" => Output <= "0100100"; --2
            when "0011" => Output <= "0110000"; --3
            when "0100" => Output <= "0011001"; --4
            when "0101" => Output <= "0010010"; --5
            when "0110" => Output <= "0000010"; --6
            when "0111" => Output <= "1111000"; --7
            when "1000" => Output <= "0000000"; --8
            when "1001" => Output <= "0010000"; --9
            when "1010" => Output <= "0100000"; --10 A
            when "1011" => Output <= "0000011"; --11 B
            when "1100" => Output <= "1000110"; --12 C
            when "1101" => Output <= "0100001"; --13 D
            when "1110" => Output <= "0000110"; --14 E
            when "1111" => Output <= "0001110"; --15 F
        end case;
    end process;
end Behavioral;
```


TOPLEVEL

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity TopLevel is
    port(Ao,Bo : in std_logic_vector(3 downto 0);
         SELo : in std_logic_vector(1 downto 0);
         OUTPUTo: out std_logic_vector (6 downto 0));--for display
end TopLevel;

architecture Behavioral of TopLevel is
    signal ALU_OUT_DISPLAY_IN : std_logic_vector(3 downto 0);--signal for the output of the
    ALU which is also the input for the Display

    --ALU component
    component ALU port(A,B : in std_logic_vector(3 downto 0);
                      SEL : in std_logic_vector(1 downto 0);
                      OUTPUT: out std_logic_vector (3 downto 0));
    end component;

    component Display port(Input :in std_logic_vector(3 downto 0);
                          Output :out std_logic_vector(6 downto 0));
    end component;

begin

    TopALU : ALU port
    map(A=>Ao,B=>Bo,SEL=>SELo,OUTPUT=>ALU_OUT_DISPLAY_IN);
    TopDisplay : Display port map(Input=>ALU_OUT_DISPLAY_IN,Output=>OUTPUTo);

end Behavioral;
```

CONSTRAINT FILES

```
set_property IOSTANDARD LVCMOS33 [get_ports {Ao[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Ao[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Ao[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Ao[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Bo[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Bo[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Bo[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Bo[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {OUTPUTo[6]}]
set_property IOSTANDARD LVCMOS33 [get_ports {OUTPUTo[5]}]
set_property IOSTANDARD LVCMOS33 [get_ports {OUTPUTo[4]}]
set_property IOSTANDARD LVCMOS33 [get_ports {OUTPUTo[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {OUTPUTo[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {OUTPUTo[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {OUTPUTo[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {SELo[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {SELo[0]}]
set_property PACKAGE_PIN W17 [get_ports {Ao[3]}]
set_property PACKAGE_PIN W16 [get_ports {Ao[2]}]
set_property PACKAGE_PIN V16 [get_ports {Ao[1]}]
set_property PACKAGE_PIN V17 [get_ports {Ao[0]}]
set_property PACKAGE_PIN R2 [get_ports {Bo[3]}]
set_property PACKAGE_PIN T1 [get_ports {Bo[2]}]
set_property PACKAGE_PIN U1 [get_ports {Bo[1]}]
set_property PACKAGE_PIN W2 [get_ports {Bo[0]}]
set_property PACKAGE_PIN U7 [get_ports {OUTPUTo[6]}]
set_property PACKAGE_PIN V5 [get_ports {OUTPUTo[5]}]
set_property PACKAGE_PIN U5 [get_ports {OUTPUTo[4]}]
set_property PACKAGE_PIN V8 [get_ports {OUTPUTo[3]}]
set_property PACKAGE_PIN U8 [get_ports {OUTPUTo[2]}]
set_property PACKAGE_PIN W6 [get_ports {OUTPUTo[1]}]
set_property PACKAGE_PIN W7 [get_ports {OUTPUTo[0]}]
set_property PACKAGE_PIN W13 [get_ports {SELo[1]}]
set_property PACKAGE_PIN W14 [get_ports {SELo[0]}]
```

PART 2

FSM

```
library ieee;
use ieee. std_logic_1164.all;
use ieee. std_logic_arith.all;
use ieee. std_logic_unsigned.all;
```

Entity FSM is--With Feedback

```
Port(RESET, CLK, INPUT: in std_logic;
      OUTPUT: out std_logic_vector(1 downto 0));
```

End;

Architecture Behavioral of FSM is

```
Signal CS,NS: std_logic_vector(1 downto 0); --Current and Next State
```

```
Begin
```

```
Process(RESET,CLK)
```

```
Begin
```

```
    if (RESET = '1')then-- When RESET is active
```

```
        CS<= "00";--Reset State Machine
```

```
    elsif(CLK='1' and CLK'EVENT) then
```

```
        CS<=NS;--When Clock is active, move to next state
```

```
    end if;
```

```
end process;
```

```
process (CS,INPUT)
```

```
begin
```

```
case CS is
```

```
when ("00")=>--State 0
```

```
    if (INPUT = '1') then
```

```
        NS<= "01";
```

```
    else
```

```
        NS <= CS; --Stay in State
```

```
    end if;
```

```
When ("01")=>--State 1
```

```
    if (INPUT = '1') then
```

```
        NS<= "10";
```

```
    else
```

```
        NS <= CS; --Stay in State
```

```
    end if;
When ("10")=>--State 2
    if (INPUT = '1') then
        NS<= "11";
    else
        NS <= CS; --Stay in State
    end if;
When ("11")=>--State 3
    if (INPUT = '1') then
        NS<= "00";
    else
        NS <= CS; --Stay in State
    end if;
end case;
end process;
OUTPUT<= CS;
end Behavioral;
```


CLOCK DIVIDER

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity ClockDivider is
    port( clk : in STD_LOGIC ;
          RESET : in STD_LOGIC ;
          SlowClock , led0 : out STD_LOGIC );
end Clockdivider ;

architecture beh of Clockdivider is
    --signals for clock
    signal slowClock_sig : STD_LOGIC;
    begin
        process

            variable cnt : STD_LOGIC_VECTOR (26 downto 0):= "00000000000000000000000000000000"
; --Counter. When this variable reaches the Most Significant Bit approximatley one second (1
Hz) will have passed

            begin
                wait until (( clk 'EVENT) AND ( clk = '1')) ;--Wait until clock is high

                if ( RESET = '1') then
                    --Reset the Counter
                    cnt := "00000000000000000000000000000000" ;
                else
                    --Start Counting by incrementing by 1
                    cnt := STD_LOGIC_VECTOR( unsigned ( cnt ) + 1);
                end if ;

                SlowClock  <= cnt (26);      --SlowClock = 1Hz
                slowClock_sig <= cnt (26);    -- same as slow clock

                --Display the clock information to the LED
                if ( slowClock_sig = '1') then
                    led0 <= '1';
```

```

        else
            led0 <= '0';
        end if;

    end process;
end beh;

```

DISPLAY

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Display is
    port(Input :in std_logic_vector(1 downto 0);
         Output :out std_logic_vector(6 downto 0));
end Display;

architecture Behavioral of Display is
    begin
        process (Input)
        begin
            case Input is
                --Individual Segments
                when "00" => Output <= "1000000"; --0
                when "01" => Output <= "1111001"; --1
                when "10" => Output <= "0100100"; --2
                when "11" => Output <= "0110000"; --3
            end case;
        end process;
    end Behavioral;

```

TOPLEVEL

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity TopLevel is
    port(CLKo,RESETo,INPUTo : in std_logic;
        CommandLed : out std_logic_vector(1 downto 0);--Shows Command on State Machine
        (for ALU even though not used in part 2)
        CLKled : out std_logic;--Shows Clock
        OUTPUTo: out std_logic_vector (6 downto 0));--Shows State
end TopLevel;

architecture Behavioral of TopLevel is
    signal CommandTemp : std_logic_vector(1 downto 0);
    signal SlowClockTemp : std_logic;

    --FSM component
    component FSM is port(RESET, CLK, INPUT: in std_logic;
        OUTPUT: out std_logic_vector(1 downto 0));
    end component;

    --Clock component
    component ClockDivider is port( clk : in STD_LOGIC ;
        RESET : in STD_LOGIC ;
        SlowClock , led0 : out STD_LOGIC );
    end component;

    --Display component
    component Display port(Input :in std_logic_vector(1 downto 0);
        Output :out std_logic_vector(6 downto 0));
    end component;

begin

    TopFSM : FSM port map(RESET=>RESETo, CLK=> SlowClockTemp, INPUT=> INPUTo,
        OUTPUT=>CommandTemp);

    TopClock : ClockDivider port map(CLK=>CLKo, RESET=> RESETo,SlowClock =>
        SlowClockTemp, led0=>CLKled );

    TopDisplay : Display port map(Input=>CommandTemp, Output=>OUTPUTo);
```

CommandLed <= CommandTemp; --Sends the value of the command (output of FSM) to the LED

end Behavioral;

CONSTRAINT FILE

```
set_property IOSTANDARD LVCMOS33 [get_ports {CommandLed[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {CommandLed[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {OUTPUTo[6]}]
set_property IOSTANDARD LVCMOS33 [get_ports {OUTPUTo[5]}]
set_property IOSTANDARD LVCMOS33 [get_ports {OUTPUTo[4]}]
set_property IOSTANDARD LVCMOS33 [get_ports {OUTPUTo[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {OUTPUTo[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {OUTPUTo[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {OUTPUTo[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports CLKled]
set_property IOSTANDARD LVCMOS33 [get_ports CLKo]
set_property IOSTANDARD LVCMOS33 [get_ports INPUTo]
set_property IOSTANDARD LVCMOS33 [get_ports RESETo]
set_property PACKAGE_PIN L1 [get_ports {CommandLed[1]}]
set_property PACKAGE_PIN P1 [get_ports {CommandLed[0]}]
set_property PACKAGE_PIN U7 [get_ports {OUTPUTo[6]}]
set_property PACKAGE_PIN V5 [get_ports {OUTPUTo[5]}]
set_property PACKAGE_PIN U5 [get_ports {OUTPUTo[4]}]
set_property PACKAGE_PIN V8 [get_ports {OUTPUTo[3]}]
set_property PACKAGE_PIN U8 [get_ports {OUTPUTo[2]}]
set_property PACKAGE_PIN W6 [get_ports {OUTPUTo[1]}]
set_property PACKAGE_PIN W7 [get_ports {OUTPUTo[0]}]
set_property PACKAGE_PIN V3 [get_ports CLKled]
set_property PACKAGE_PIN W5 [get_ports CLKo]
set_property PACKAGE_PIN R2 [get_ports INPUTo]
set_property PACKAGE_PIN T1 [get_ports RESETo]
```


PART 3

ALU

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
use ieee.numeric_std.all;
```

entity ALU is

```
    generic ( constant X: natural := 3); --for shifts and roates, number of bits is 3
    port(A,B : in std_logic_vector(3 downto 0);
         SEL : in std_logic_vector(1 downto 0);
         OUTPUT: out std_logic_vector (3 downto 0));
```

end;

architecture Behavioral of ALU is

signal OutTemp, XOROutTemp : std_logic_vector(3 downto 0); --holds value for output of A and B XORED, which will be shifted. Also a regular output temp signal

```
    begin
    process(SEL)
    begin
        if(SEL = "00") then
            OutTemp <= A XOR B; --XOR
            XOROutTemp <= OutTemp;
        elsif(SEL = "01") then
            OutTemp <= A NAND B; --NAND
        elsif(SEL = "10") then
            OutTemp <= (A NAND B) + "0100"; --ADD 4 to the inputs Nanded
            --OutTemp <= std_logic_vector(unsigned(XOROutTemp) sll X);--Shift Left
        elsif(SEL = "11") then
            OutTemp <= (A NAND B) - "0010"; --SUBTRACT 2 to the inputs Nanded
            --OutTemp <= std_logic_vector(unsigned(XOROutTemp) srl X);--Shift Right
        end if;
    end process;
    OUTPUT <= OutTemp;
end Behavioral;
```

FSM

```
library ieee;
use ieee. std_logic_1164.all;
use ieee. std_logic_arith.all;
use ieee. std_logic_unsigned.all;
```

Entity FSM is

```
Port(RESET, CLK, INPUT: in std_logic;
      OUTPUT: out std_logic_vector(1 downto 0));
```

End;

Architecture Behavioral of FSM is

```
Signal CS,NS: std_logic_vector(1 downto 0); --Current and Next State
```

```
Begin
```

```
Process(RESET,CLK)
```

```
Begin
```

```
    if (RESET = '1')then-- When RESET is active
```

```
        CS<= "00";--Reset State Machine
```

```
    elsif(CLK='1' and CLK'EVENT) then
```

```
        CS<=NS;--When Clock is active, move to next state
```

```
    end if;
```

```
end process;
```

```
process (CS,INPUT)
```

```
begin
```

```
case CS is
```

```
when ("00")=>--State 0
```

```
    if (INPUT = '1') then
```

```
        NS<= "01";
```

```
    else
```

```
        NS <= CS; --Stay in State
```

```
    end if;
```

```
When ("01")=>--State 1
```

```
    if (INPUT = '1') then
```

```
        NS<= "10";
```

```
    else
```

```
        NS <= CS; --Stay in State
```

```
    end if;
```

```
When ("10")=>--State 2
```

```
    if (INPUT = '1') then
        NS<= "11";
    else
        NS <= CS; --Stay in State
    end if;
When ("11")=>--State 3
    if (INPUT = '1') then
        NS<= "00";
    else
        NS <= CS; --Stay in State
    end if;
end case;
end process;
OUTPUT<= CS;
end Behavioral;
```

CLOCK DIVIDER

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity ClockDivider is
    port( clk : in STD_LOGIC ;
          RESET : in STD_LOGIC ;
          SlowClock , led0 : out STD_LOGIC );
end Clockdivider ;

architecture beh of Clockdivider is
    --signals for clock
    signal slowClock_sig : STD_LOGIC;
    begin
        process

            variable cnt : STD_LOGIC_VECTOR (26 downto 0):= "00000000000000000000000000000000"
; --Counter. When this variable reaches the Most Significant Bit approximatley one second (1
Hz) will have passed

            begin
                wait until (( clk 'EVENT) AND ( clk = '1')) ;--Wait until clock is high

                if ( RESET = '1') then
                    --Reset the Counter
                    cnt := "00000000000000000000000000000000" ;
                else
                    --Start Counting by incrementing by 1
                    cnt := STD_LOGIC_VECTOR( unsigned ( cnt ) + 1);
                end if ;

                SlowClock  <= cnt (26);      --SlowClock = 1Hz
                slowClock_sig <= cnt (26);    -- same as slow clock

                --Display the clock information to the LED
                if ( slowClock_sig = '1') then
                    led0 <= '1';
```

```
        else
            led0 <= '0';
        end if;

    end process;
end beh;
```


DISPLAY

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Display is
    port(Input :in std_logic_vector(3 downto 0);
         Output :out std_logic_vector(6 downto 0));
end Display;
```

architecture Behavioral of Display is

```
begin
    process (Input)
    begin
        case Input is
            --Individual Segments
            when "0000" => Output <= "1000000"; --0
            when "0001" => Output <= "1111001"; --1
            when "0010" => Output <= "0100100"; --2
            when "0011" => Output <= "0110000"; --3
            when "0100" => Output <= "0011001"; --4
            when "0101" => Output <= "0010010"; --5
            when "0110" => Output <= "0000010"; --6
            when "0111" => Output <= "1111000"; --7
            when "1000" => Output <= "0000000"; --8
            when "1001" => Output <= "0010000"; --9
            when "1010" => Output <= "0100000"; --10 A
            when "1011" => Output <= "0000011"; --11 B
            when "1100" => Output <= "1000110"; --12 C
            when "1101" => Output <= "0100001"; --13 D
            when "1110" => Output <= "0000110"; --14 E
            when "1111" => Output <= "0001110"; --15 F
        end case;
    end process;
end Behavioral;
```

TOP LEVEL

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity TopLevel is
    port(Ao,Bo : in std_logic_vector(3 downto 0);--Inputs for ALU
        FSMIn : in std_logic;--Input for FSM
        CLKo,RESETo : in std_logic;
        CLKled : out std_logic;--Shows Clock
        StateLED : out std_logic_vector(1 downto 0); --Shows the current State, the output of the
FSM
        OUTPUTo: out std_logic_vector (6 downto 0));--for display, shows result of ALU
end TopLevel;
```

architecture Behavioral of TopLevel is

```
    signal FSMoutTemp : std_logic_vector(1 downto 0); --The command of the FSM which is
used as the select bit of the ALU
    signal ALUoutTemp : std_logic_vector(3 downto 0); --The output of the ALU which will be
used as the input of the 7SegDisplay
    signal SlowClockTemp : std_logic; --For the SlowClock
```

--ALU component

```
component ALU port(A,B : in std_logic_vector(3 downto 0);
    SEL : in std_logic_vector(1 downto 0);
    OUTPUT: out std_logic_vector (3 downto 0));
end component;
```

--Display Component

```
component Display port(Input :in std_logic_vector(3 downto 0);
    Output :out std_logic_vector(6 downto 0));
end component;
```

--FSM component

```
component FSM is port(RESET, CLK, INPUT: in std_logic;
    OUTPUT: out std_logic_vector(1 downto 0));
end component;
```

--Clock component

```
component ClockDivider is port( clk : in STD_LOGIC ;
    RESET : in STD_LOGIC ;
    SlowClock , led0 : out STD_LOGIC );
```

```
end component;
```

```
begin
```

```
    TopALU : ALU port map(A=>Ao, B=>Bo, SEL=> FSMoutTemp, OUTPUT=>ALUoutTemp  
);
```

```
    TopDisplay : Display port map(Input=> ALUoutTemp, Output=>OUTPUTo);
```

```
    TopFSM : FSM port map(RESET=>RESETo, CLK=>SlowClockTemp, INPUT=> FSMin,  
OUTPUT=>FSMoutTemp);
```

```
    TopClock : ClockDivider port map(clk=>CLKo, RESET=>RESETo,SlowClock =>  
SlowClockTemp, led0=>CLKled );
```

```
    StateLED <= FSMoutTemp;
```

```
end Behavioral;
```

CONSTRAINT FILES

```
set_property IOSTANDARD LVCMOS33 [get_ports {Ao[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Ao[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Ao[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Ao[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Bo[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Bo[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Bo[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Bo[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {OUTPUTo[6]}]
set_property IOSTANDARD LVCMOS33 [get_ports {OUTPUTo[5]}]
set_property IOSTANDARD LVCMOS33 [get_ports {OUTPUTo[4]}]
set_property IOSTANDARD LVCMOS33 [get_ports {OUTPUTo[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {OUTPUTo[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {OUTPUTo[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {OUTPUTo[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {StateLED[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {StateLED[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports CLKled]
set_property IOSTANDARD LVCMOS33 [get_ports CLKo]
set_property IOSTANDARD LVCMOS33 [get_ports FSMin]
set_property IOSTANDARD LVCMOS33 [get_ports RESETo]
set_property PACKAGE_PIN W17 [get_ports {Ao[3]}]
set_property PACKAGE_PIN W16 [get_ports {Ao[2]}]
set_property PACKAGE_PIN V16 [get_ports {Ao[1]}]
set_property PACKAGE_PIN V17 [get_ports {Ao[0]}]
set_property PACKAGE_PIN R2 [get_ports {Bo[3]}]
set_property PACKAGE_PIN T1 [get_ports {Bo[2]}]
set_property PACKAGE_PIN U1 [get_ports {Bo[1]}]
set_property PACKAGE_PIN W2 [get_ports {Bo[0]}]
set_property PACKAGE_PIN U7 [get_ports {OUTPUTo[6]}]
set_property PACKAGE_PIN V5 [get_ports {OUTPUTo[5]}]
set_property PACKAGE_PIN U5 [get_ports {OUTPUTo[4]}]
set_property PACKAGE_PIN V8 [get_ports {OUTPUTo[3]}]
set_property PACKAGE_PIN U8 [get_ports {OUTPUTo[2]}]
set_property PACKAGE_PIN W6 [get_ports {OUTPUTo[1]}]
set_property PACKAGE_PIN W7 [get_ports {OUTPUTo[0]}]
set_property PACKAGE_PIN E19 [get_ports {StateLED[1]}]
set_property PACKAGE_PIN U16 [get_ports {StateLED[0]}]
```

```
set_property PACKAGE_PIN V3 [get_ports CLKled]  
set_property PACKAGE_PIN W5 [get_ports CLKo]  
set_property PACKAGE_PIN T3 [get_ports FSMin]  
set_property PACKAGE_PIN V2 [get_ports RESETo]
```