

ECEN 429: Introduction to Digital Systems Design Laboratory
North Carolina Agricultural and Technical State University
Department of Electrical and Computer Engineering

Ian Parker (Reporter)

Tayanna Lee (Lab Partner)


April 18, 2019

Lab #9

Introduction: For lab 9, we continue to implement FSM. This time we used the function of a finite state machine to control traffic lights. The components include: North/South lights, East/West lights, a N/S and E/W turn lane light and sensor and a crosswalk (w/o buttons in Part 1 and with buttons for Part 2).



Background

Overall Finite State Machine for traffic light implementation:

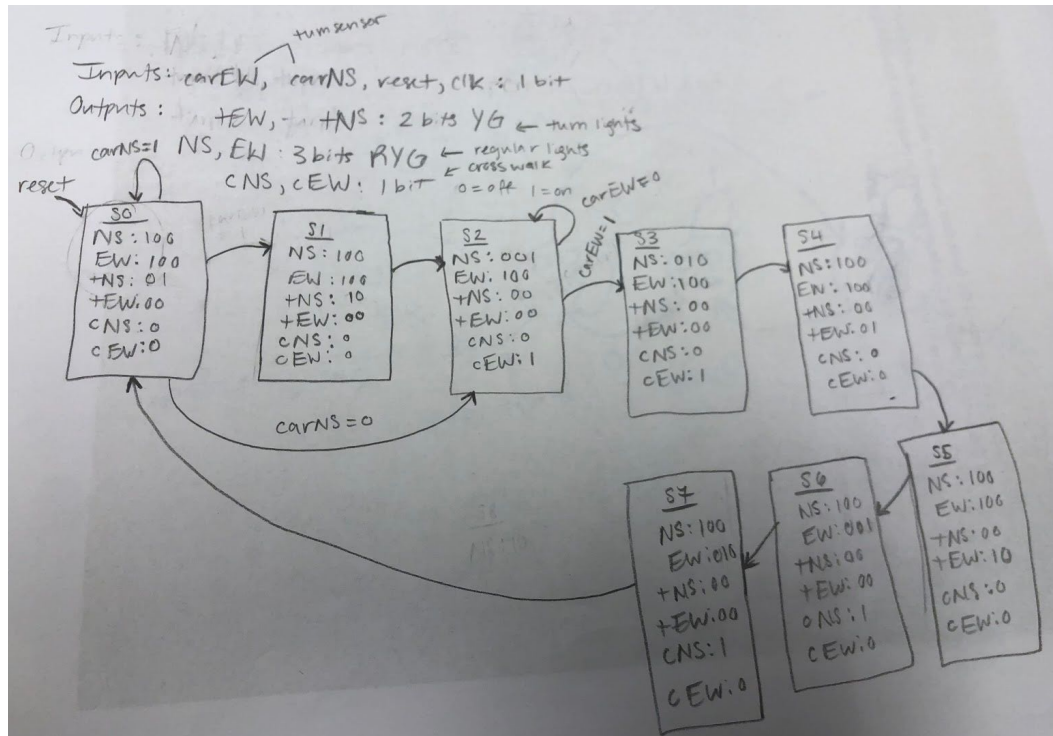


Part 1

State Diagram

  

Schematic

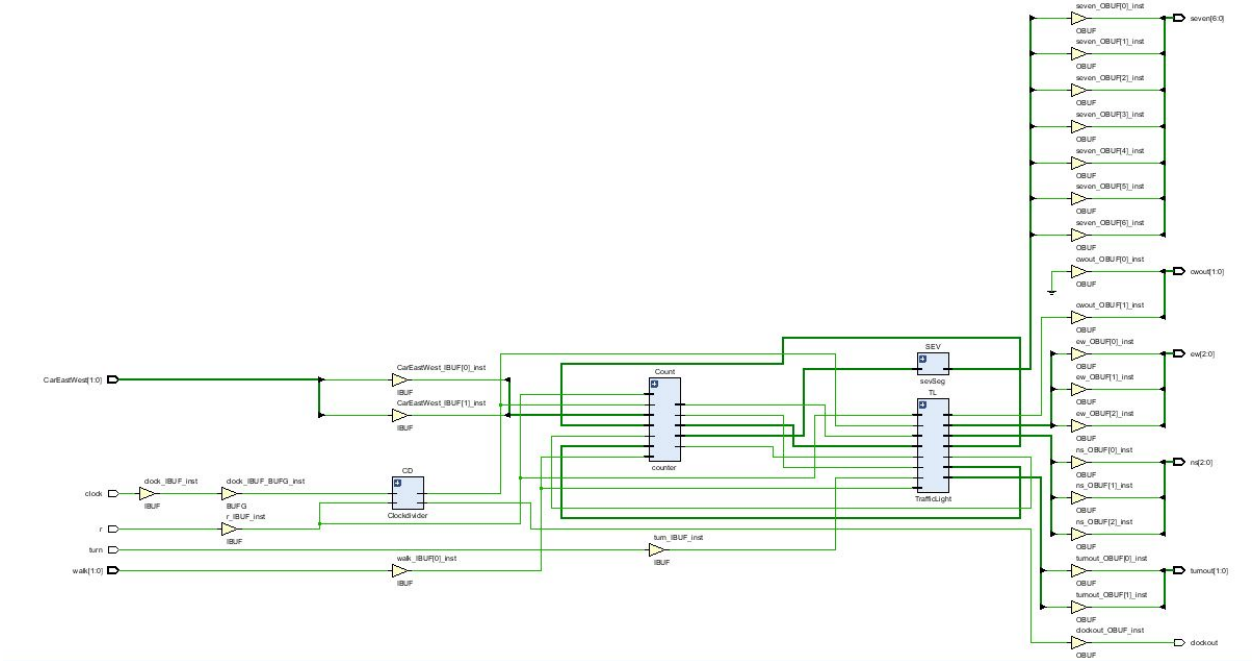

Pin Assignments

CarEastWest (2)	IN							✓
CarEastWest[1]	IN					R2	✓	✓
CarEastWest[0]	IN					T1	✓	✓
cwout (2)	OUT						✓	✓
cwout[1]	OUT					P3	✓	✓
cwout[0]	OUT					U16	✓	✓
ew (3)	OUT						✓	✓
ew[2]	OUT					L1	✓	✓
ew[1]	OUT					P1	✓	✓
ew[0]	OUT					N3	✓	✓
ns (3)	OUT						✓	✓
ns[2]	OUT					V19	✓	✓
ns[1]	OUT					U19	✓	✓
ns[0]	OUT					E19	✓	✓
seven (7)	OUT						✓	✓
seven[6]	OUT					W7	✓	✓
seven[5]	OUT					W6	✓	✓
seven[4]	OUT					U8	✓	✓
seven[3]	OUT					V8	✓	✓
seven[2]	OUT					U5	✓	✓
seven[1]	OUT					V5	✓	✓
seven[0]	OUT					U7	✓	✓
turnout (2)	OUT						✓	✓
turnout[1]	OUT					V14	✓	✓
turnout[0]	OUT					U14	✓	✓
walk (2)	IN						✓	✓
walk[1]	IN					W2	✓	✓
walk[0]	IN					R3	✓	✓
Scalar ports (4)								
clock	IN					W5	✓	✓
clockout	OUT					V3	✓	✓
r	IN					U1	✓	✓
turn	IN					V7	✓	✓

Results

 


Figure 1.1) Reset State to North South on Green



 


Figure 1.2) A car is in the east west lane triggering a signal to turn North South light from Green->Yellow->Red

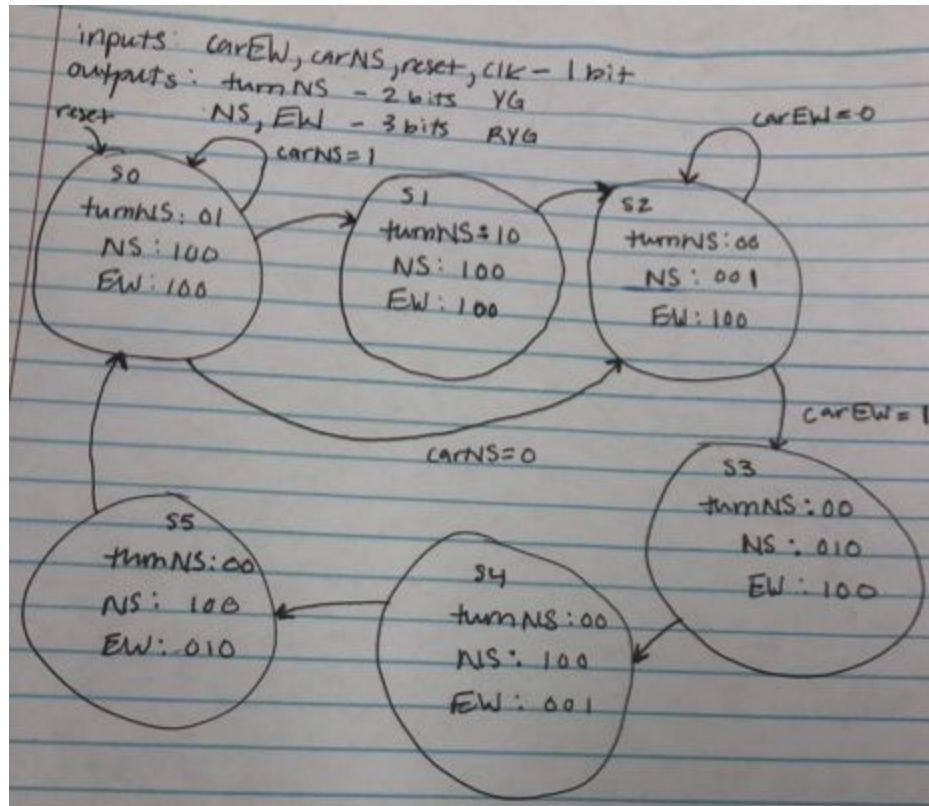

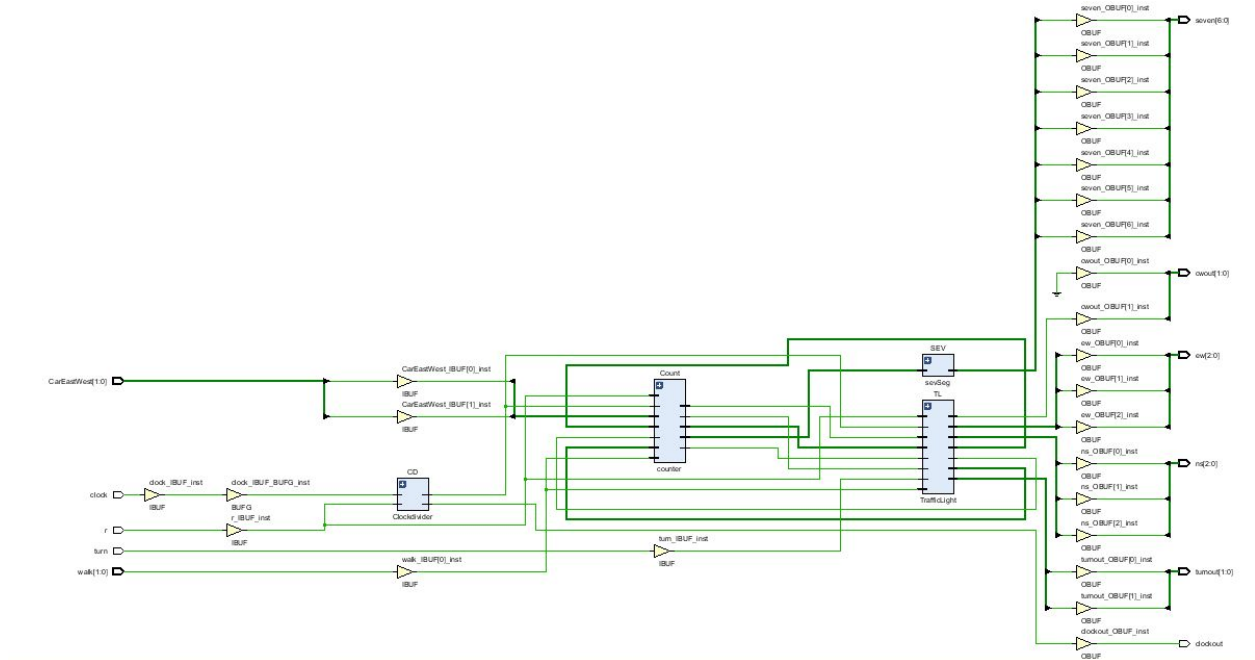












 

















Part2 State Diagram

 

Schematic

 

 Pin Assignments

▼  CarEastWest (2)	IN						✓
 CarEastWest[1]	IN				R2	▼	✓
 CarEastWest[0]	IN				T1	▼	✓
▼  cwout (2)	OUT						✓
 cwout[1]	OUT				P3	▼	✓
 cwout[0]	OUT				U16	▼	✓
▼  ew (3)	OUT						✓
 ew[2]	OUT				L1	▼	✓
 ew[1]	OUT				P1	▼	✓
 ew[0]	OUT				N3	▼	✓
▼  ns (3)	OUT						✓
 ns[2]	OUT				V19	▼	✓
 ns[1]	OUT				U19	▼	✓
 ns[0]	OUT				E19	▼	✓
▼  seven (7)	OUT						✓
 seven[6]	OUT				W7	▼	✓
 seven[5]	OUT				W6	▼	✓
 seven[4]	OUT				U8	▼	✓
 seven[3]	OUT				V8	▼	✓
 seven[2]	OUT				U5	▼	✓
 seven[1]	OUT				V5	▼	✓
 seven[0]	OUT				U7	▼	✓
▼  turnout (2)	OUT						✓
 turnout[1]	OUT				V14	▼	✓
 turnout[0]	OUT				U14	▼	✓
▼  walk (2)	IN						✓
 walk[1]	IN				W2	▼	✓
 walk[0]	IN				R3	▼	✓
▼  Scalar ports (4)							
 clock	IN				W5	▼	✓
 clockout	OUT				V3	▼	✓
 r	IN				U1	▼	✓
 turn	IN				V7	▼	✓

Results

 


Figure 2.1) Crosswalk button has been pressed and count yet to start because there is still traffic

 


Figure 2.2) No input signals from east west or crosswalk so light as remains at North South Green

Conclusion: With this lab, we continued our deep learning about finite state machines and how to perform advance implementations. As mentioned before, we used a FSM to control traffic lights that include turning sensors and crosswalk buttons. We learn how to implement the FSM, Seven-segment display, and clock divider.

Appendices :

Part 1 VHDL TopLevel

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
```

entity TopLevel is

```
Port (CarEastWest,walk: in std_logic_vector(1 downto 0);
      clock,r,turn:in std_logic;
      clockout: out std_logic;
      turnout, cwout: out std_logic_vector(1 downto 0);--turn signal and cross walk
      ns,ew:out std_logic_vector(2 downto 0);--lights for NortSouth and EastWest
      seven : out std_logic_vector(6 downto 0));--seven seg display
end TopLevel;
```

architecture Behavioral of TopLevel is

```
signal tmpclk,tmpcross: std_logic;
signal tmpC1,tmpC5,crossOut,countcrosstmp: std_logic_vector(3 downto 0);
signal tmpSel,tmpwalk: std_logic_vector(1 downto 0);
```

--Traffic Light Component dec

```
component TrafficLight port (clk,reset,turn:in std_logic;
                             c1,c5,countcross:in std_logic_vector(3 downto 0);--counters to one second and 5 seconds
                             cew: in std_logic_vector(1 downto 0);--car in the east west lane signal
                             cwin : in std_logic_vector(1 downto 0);--cross walk input (button pressed) in NS and EW
                             cwout: out std_logic_vector(1 downto 0);-- cross walk output (g or not) in NS and EW
                             csel : out std_logic;
                             sel,turnsig,crosswalk: out std_logic_vector(1 downto 0);--select bit and turn signal
                             northsouth,eastwest:out std_logic_vector(2 downto 0));
```

end component;

--Counter Component dec

```
component counter port(clk,reset:in std_logic;
                       input:in std_logic_vector(1 downto 0);
                       crosser : in std_logic;
                       c1,c5,crossOut:out std_logic_vector(3 downto 0));
```

end component;

--ClockDivider Component dec

```
component clockdivider port(clk : in STD_LOGIC;
                             reset : in STD_LOGIC;
                             SlowClock,ledO : out STD_LOGIC);
```

end component;

--Seven Segment Display Component dec

```
component sevSeg port(input: in std_logic_vector (3 downto 0);
                      output:out std_logic_vector(6 downto 0));
```

end component;

begin

--Instantiation

CD: clockdivider port map(clk=>clock,reset=>r,SlowClock=>tmpclk,ledO=>clockout);

TL: TrafficLight port

```
map(clk=>tmpclk,reset=>r,turn=>turn,c1=>tmpc1,c5=>tmpc5,countcross=>countcrosstmp,cew=>CarEastWest,cwin=>walk,cwout=>cwout,csel=>tmpcross,sel=>tmpSel,turnsig=>turnout,northsouth=>ns,eastwest=>ew);
```

```
    Count: counter port map (clk=>tmpclk,reset=>r,input=>tmpSel,crosser=>tmpercross,  
c1=>tmpe1,c5=>tmpe5,crossout=>countcrosstmp);  
    SEV: sevSeg port map (input=>countcrosstmp, output=>seven);  
  
end Behavioral;
```

Clock Divider

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
use ieee.std_logic_unsigned.all;
```

entity Clockdivider is

```
Port ( clk : in  STD_LOGIC;
      reset : in  STD_LOGIC;
      SlowClock,ledO : out STD_LOGIC);
end Clockdivider;
```

architecture behavioral of Clockdivider is

signal slowSig: std_logic;

begin

process

variable cnt : std_logic_vector(26 downto 0):= "0000000000000000000000000000";

begin -- calculations

wait until ((clk'EVENT) AND (clk = '1'));

if (reset = '1') then

cnt := "0000000000000000000000000000";

else

cnt := cnt + 1; -- count to 26

end if;

SlowClock <= cnt(26);

slowSig<=cnt(26);

if(slowSig='1')then

ledO<='1';

else

ledO<='0';

end if;

end process;

end Behavioral;

Traffic Light

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity TrafficLight is

```
Port (clk,reset,turn:in std_logic;
      c1,c5,countcross:in std_logic_vector(3 downto 0);--counters to one second and 5 seconds and for the cross
walk
      cew: in std_logic_vector(1 downto 0);--car in the east west lane signal
      cwin : in std_logic_vector(1 downto 0);--cross walk input (button pressed) in NS and EW
      cwout: out std_logic_vector(1 downto 0);-- cross walk output (g or not) in NS and EW
      csel : out std_logic;
      sel,turnsig,crosswalk : out std_logic_vector(1 downto 0);--select bit and turn signal
      northsouth,eastwest:out std_logic_vector(2 downto 0));
```

end TrafficLight;

architecture Beh of TrafficLight is

```
type state_type is (nsg,nsy,nsr,ewr,ewg,ewy,tg,ty);
signal cs,ns: state_type;
signal walk : std_logic_vector(1 downto 0);

begin
process(clk,reset)
begin
    if (reset='1')then
        cs<=nsg;
    elsif(clk'event and clk='1')then
        cs<=ns;
    end if;
end process;

process(cs,cew)
begin
    turnsig <="00";
    crosswalk<= "00";
    csel <= '0';
    case cs is
        when nsg =>--north south green
            --outputs of this state
            northsouth <= "001";--green
            eastwest <= "100";--red

            sel<="10"; --count to 5
            if(cwin = "01" or cwin = "11") then
                cSel<= '1';
            end if;
            if(c5="0101" and (cew="01" or cew="10" or cew="11" or cwin = "00" or cwin ="01" or cwin="10" or
cwin="11")) then-- no crosswalk input or east west cross input or ignore
                ns<=nsy;
            else
                ns<=cs;
            end if;
        end case;
    end process;
```

```

end if;

when nsy =>--north south yellow
  --outputs of this state
  northsouth <= "010";--yellow
  eastwest <= "100";--red
  sel<="01"; --count to 1
  --cwout<= "01";--walk in NS
  walk<= "10";
  if(c1="0001") then
    ns <= nsr;
  end if;
when nsr =>--north south red
  --outputs of this state
  northsouth <= "100";--red
  eastwest <= "100";--red
  sel<="01"; --count to 1
  --cwout<= "00";-- no walking
  if (c1 = "0001" and (cew="01" or cew ="10" or cew="11" or cwin = "00" or cwin ="01" or cwin="10"
or cwin="11" ))then
    ns <= ewg;
  elseif(c1="0001" and turn = '1' and cew="00") then
    ns<= tg;
  end if;

when ewg =>--east west green
  --outputs of this state
  northsouth <= "100";--red
  eastwest <= "001";--green
  sel<="10"; --count to 5
  walk<="01";
  --cwout<= "01"; --walk in EW
  if(walk<="01" and (cwin = "01" or cwin = "11")) then -- no cross input or north south cross input or
ignore
    csel<='1';
    crosswalk<="01";
    if(countercross="0110" )then
      crosswalk<= "01";
    end if;
  end if;

  if(c5="0101" and (cew="00" or cwin="01" or cwin="11")) then
    ns<=ewy;
  else
    ns<=cs;
  end if;
when ewy =>--easy west yellow
  --outputs of this state

```

```

        northsouth <= "100";--red
        eastwest <= "010";--yellow
        sel<="01"; --count to 1
        cwout<= "10"; --walk in ew
        if(c1="0001") then
            ns <= ewr;
        end if;
    when ewr =>--east west red
        --outputs of this state
        northsouth <= "100";--red
        eastwest <= "100";--red
        sel<="01"; --count to 1
        cwout<= "00";---no walking
        if(c1="0001" and turn ='1') then
            ns <= tg;
        elsif(c1="0001" and (turn ='0' or cwin="10" or cwin="11"))then
            ns<=nsg;
        end if;
    when tg =>--turn green
        --outputs of this state
        turnsig<= "10"; --turnsig signal light is green
        northsouth <= "100";--red
        eastwest <= "100";--red
        sel<="10"; --count to 5
        cwout<= "00";--no walking
        if(c5="0101")then
            ns <= ty;
        else
            ns<= cs;
        end if;
    when ty =>--turn yellow
        --outputs of this state
        turnsig <="01"; --turnsig signal light is yellow
        northsouth <= "100";--red
        eastwest <= "100";--red
        sel<="01"; --count to 1
        cwout<= "00"; --no walking
        if(c1="0001") then
            ns <= nsg;
        else
            ns<=cs;
        end if;

end case;
end process;
end Beh;

```

Counter

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
use ieee.std_logic_unsigned.all;
```


entity counter is

```
Port (clk,reset:in std_logic;
      input:in std_logic_vector(1 downto 0);
      crosser : in std_logic;--person needs to cross street
      c1,c5, crossOut :out std_logic_vector(3 downto 0));--count to 1 and count to 5
end counter;
```

architecture Behavioral of counter is

```
    signal tmp1,tmp2, crossertemp : std_logic_vector(3 downto 0);--counter signals

begin

    process(reset,clk)
    begin
        tmp1<="0000";
        tmp2<="0000";
        crossertemp<="0000";
        if(reset='1')then
            --reset counts
            tmp1<="0000";
            tmp2<="0000";
        elsif(clk'event and (clk='1'))then--on the rising edge
            if(input = "01")then
                if(tmp1 < 2) then --count to 1 (0,1)
                    tmp1 <= tmp1 + "0001";
                end if;
            elsif(input="10")then
                if(tmp2 < 5)then --count to 5 (0,1,2,3,4)
                    tmp2 <= tmp2 + "0001";
                end if;
            end if;
            if(crosser = '1')then
                if(crossertemp<6)then
                    crossertemp<= crossertemp + "0001";
                end if;
            end if;
            --set the values
            c1 <= tmp1;
            c5 <=tmp2;
            crossOut <= crossertemp;
        end process;
    end Behavioral;
```

Seven Segment Display

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
use ieee.std_logic_unsigned.all;
```

```
entity sevSeg is
  Port (input: in std_logic_vector (3 downto 0);
        output:out std_logic_vector(6 downto 0));-- lsb
end ;
```

architecture Behavioral of sevSeg is

```
begin
process(input)
begin
case input is
when "0000" =>
  output <= "1000000"; --0
when "0001" =>
  output <= "1111001"; --1
when "0010" =>
  output <= "0100100";--2
when "0011" =>
  output <= "0110000"; --3
when "0100" =>
  output <= "0011001"; --4
when "0101" =>
  output <= "0010010";--5
when "0110" =>
  output <= "0000010";--6
when "0111" =>
  output <= "1111000";--7
when "1000" =>
  output <= "0000000";--8
when "1001" =>
  output <= "0010000";--9
when "1010" =>
  output <= "0100000";--10 A
when "1011" =>
  output <= "0000011";--11 B
when "1100" =>
  output <= "1000110";--12 C
when "1101" =>
  output <= "0100001";--13 D
when "1110" =>
  output <= "0000110";--14 E
when "1111" =>
  output <= "0001110";--15 F
end case;
end process;
```

end Behavioral;

Constraints

```
set_property IOSTANDARD LVCMOS33 [get_ports {CarEastWest[1]}]  
set_property IOSTANDARD LVCMOS33 [get_ports {CarEastWest[0]}]  
set_property IOSTANDARD LVCMOS33 [get_ports {ew[2]}]  
set_property IOSTANDARD LVCMOS33 [get_ports {ew[1]}]
```



```
set_property IOSTANDARD LVCMOS33 [get_ports {ew[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {ns[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {ns[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {ns[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {turnout[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {turnout[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports clock]
set_property IOSTANDARD LVCMOS33 [get_ports clockout]
set_property IOSTANDARD LVCMOS33 [get_ports r]
set_property PACKAGE_PIN L1 [get_ports {ew[2]}]
set_property PACKAGE_PIN P1 [get_ports {ew[1]}]
set_property PACKAGE_PIN N3 [get_ports {ew[0]}]
set_property PACKAGE_PIN V19 [get_ports {ns[2]}]
set_property PACKAGE_PIN U19 [get_ports {ns[1]}]
set_property PACKAGE_PIN E19 [get_ports {ns[0]}]
set_property PACKAGE_PIN V3 [get_ports clockout]
set_property PACKAGE_PIN W5 [get_ports clock]
set_property PACKAGE_PIN V14 [get_ports {turnout[1]}]
set_property PACKAGE_PIN U14 [get_ports {turnout[0]}]
set_property PACKAGE_PIN R2 [get_ports {CarEastWest[1]}]
set_property PACKAGE_PIN U1 [get_ports r]
```

```
set_property IOSTANDARD LVCMOS33 [get_ports {cwout[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {cwout[0]}]
set_property PACKAGE_PIN P3 [get_ports {cwout[1]}]
set_property PACKAGE_PIN U16 [get_ports {cwout[0]}]
```

```
set_property PACKAGE_PIN T1 [get_ports {CarEastWest[0]}]
```

```
set_property IOSTANDARD LVCMOS33 [get_ports {seven[6]}]
set_property IOSTANDARD LVCMOS33 [get_ports {seven[5]}]
set_property IOSTANDARD LVCMOS33 [get_ports {seven[4]}]
set_property IOSTANDARD LVCMOS33 [get_ports {seven[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {seven[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {seven[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {seven[0]}]
set_property PACKAGE_PIN W7 [get_ports {seven[6]}]
set_property PACKAGE_PIN W6 [get_ports {seven[5]}]
set_property PACKAGE_PIN U8 [get_ports {seven[4]}]
set_property PACKAGE_PIN V8 [get_ports {seven[3]}]
set_property PACKAGE_PIN U5 [get_ports {seven[2]}]
set_property PACKAGE_PIN V5 [get_ports {seven[1]}]
set_property PACKAGE_PIN U7 [get_ports {seven[0]}]
set_property PACKAGE_PIN W2 [get_ports {walk[1]}]
set_property PACKAGE_PIN R3 [get_ports {walk[0]}]
```

```
set_property IOSTANDARD LVCMOS33 [get_ports {walk[1]}]  
set_property IOSTANDARD LVCMOS33 [get_ports {walk[0]}]  
set_property IOSTANDARD LVCMOS33 [get_ports turn]
```

```
set_property PACKAGE_PIN V7 [get_ports turn]
```

Part 2 VHDL

TopLevel

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;
```

entity TopLevel is

```
Port (CarEastWest,walk: in std_logic_vector(1 downto 0);
      clock,r,turn:in std_logic;
      clockout: out std_logic;
      turnout, cwout: out std_logic_vector(1 downto 0);--turn signal and cross walk
      ns,ew:out std_logic_vector(2 downto 0);--lights for NortSouth and EastWest
      seven : out std_logic_vector(6 downto 0));--seven seg display
end TopLevel;
```

architecture Behavioral of TopLevel is

```
signal tmpclk,tmpcross: std_logic;
signal tmpC1,tmpC5,crossOut,countcrosstmp: std_logic_vector(3 downto 0);
signal tmpSel,tmpwalk: std_logic_vector(1 downto 0);
```

--Traffic Light Component dec

```
component TrafficLight port (clk,reset,turn:in std_logic;
                             c1,c5,countcross:in std_logic_vector(3 downto 0);--counters to one second and 5 seconds
                             cew: in std_logic_vector(1 downto 0);--car in the east west lane signal
                             cwin : in std_logic_vector(1 downto 0);--cross walk input (button pressed) in NS and EW
                             cwout: out std_logic_vector(1 downto 0);-- cross walk output (g or not) in NS and EW
                             csel : out std_logic;
                             sel,turnsig,crosswalk: out std_logic_vector(1 downto 0);--select bit and turn signal
                             northsouth,eastwest:out std_logic_vector(2 downto 0));
```

end component;

--Counter Component dec

```
component counter port(clk,reset:in std_logic;
                       input:in std_logic_vector(1 downto 0);
                       crosser : in std_logic;
                       c1,c5,crossOut:out std_logic_vector(3 downto 0));
```

end component;

--ClockDivider Component dec

```
component clockdivider port(clk : in STD_LOGIC;
                             reset : in STD_LOGIC;
                             SlowClock,ledO : out STD_LOGIC);
```

end component;

--Seven Segment Display Component dec

```
component sevSeg port(input: in std_logic_vector (3 downto 0);
                      output:out std_logic_vector(6 downto 0));
```

end component;

begin

--Instantiation

CD: clockdivider port map(clk=>clock,reset=>r,SlowClock=>tmpclk,ledO=>clockout);

TL: TrafficLight port

map(clk=>tmpclk,reset=>r,turn=>turn,c1=>tmpc1,c5=>tmpc5,countcross=>countcrosstmp,cew=>CarEastWest,cwin=>walk,cwout=>cwout,csel=>tmpcross,sel=>tmpSel,turnsig=>turnout,northsouth=>ns,eastwest=>ew);

```
    Count: counter port map (clk=>tmpclk,reset=>r,input=>tmpSel,crosser=>tmpercross,
c1=>tmpe1,c5=>tmpe5,crossout=>countcrosstmp);
    SEV: sevSeg port map (input=>countcrosstmp, output=>seven);

end Behavioral;
```

Clock Divider

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use ieee.std_logic_unsigned.all;
```



```

entity Clockdivider is
Port ( clk : in  STD_LOGIC;
      reset : in  STD_LOGIC;
      SlowClock,ledO : out STD_LOGIC);
end Clockdivider;

architecture behavioral of Clockdivider is
signal slowSig: std_logic;
begin
  process
    variable cnt :  std_logic_vector(26 downto 0):= "000000000000000000000000";
    begin
      -- calculations
      wait until ((clk'EVENT) AND (clk = '1'));
      if (reset = '1') then
        cnt := "000000000000000000000000";
      else
        cnt := cnt + 1; -- count to 26
      end if;

      SlowClock <= cnt(26);
      slowSig<=cnt(26);

      if(slowSig='1')then
        ledO<='1';
      else
        ledO<='0';
      end if;

    end process;
end Behavioral;

```

Traffic Light

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

```

entity TrafficLight is

```
Port (clk,reset,turn:in std_logic;
      c1,c5,countcross:in std_logic_vector(3 downto 0);--counters to one second and 5 seconds and for the cross
walk
      cew: in std_logic_vector(1 downto 0);--car in the east west lane signal
      cwin : in std_logic_vector(1 downto 0);--cross walk input (button pressed) in NS and EW
      cwout: out std_logic_vector(1 downto 0);-- cross walk output (g or not) in NS and EW
      csel : out std_logic;
      sel,turnsig,crosswalk : out std_logic_vector(1 downto 0);--select bit and turn signal
      northsouth,eastwest:out std_logic_vector(2 downto 0));
```

end TrafficLight;

architecture Beh of TrafficLight is

```
type state_type is (nsg,nsy,nsr,ewr,ewg,ewy,tg,ty);
signal cs,ns: state_type;
signal walk : std_logic_vector(1 downto 0);

begin
process(clk,reset)
begin
    if (reset='1')then
        cs<=nsg;
    elsif(clk'event and clk='1')then
        cs<=ns;
    end if;
end process;

process(cs,cew)
begin
    turnsig <="00";
    crosswalk<= "00";
    csel <= '0';
    case cs is
        when nsg =>--north south green
            --outputs of this state
            northsouth <= "001";--green
            eastwest <= "100";--red

            sel<="10"; --count to 5
            if(cwin = "01" or cwin = "11") then
                cSel<= '1';
            end if;
            if(c5="0101" and (cew="01" or cew="10" or cew="11" or cwin = "00" or cwin ="01" or cwin="10" or
cwin="11")) then-- no crosswalk input or east west cross input or ignore
                ns<=nsy;
            else
```

```

        ns<=cs;
    end if;

when nsy =>--north south yellow
    --outputs of this state
    northsouth <= "010";--yellow
    eastwest <= "100";--red
    sel<="01"; --count to 1
    --cwout<= "01";--walk in NS
    walk<= "10";
    if(c1="0001") then
        ns <= nsr;
    end if;
when nsr =>--north south red
    --outputs of this state
    northsouth <= "100";--red
    eastwest <= "100";--red
    sel<="01"; --count to 1
    --cwout<= "00";-- no walking
    if (c1 = "0001" and (cew="01" or cew ="10" or cew="11" or cwin = "00" or cwin ="01" or cwin="10"
or cwin="11" ))then
        ns <= ewg;
    elseif(c1="0001" and turn = '1' and cew="00") then
        ns<= tg;
    end if;

when ewg =>--east west green
    --outputs of this state
    northsouth <= "100";--red
    eastwest <= "001";--green
    sel<="10"; --count to 5
    walk<="01";
    --cwout<= "01"; --walk in EW
    if(walk<="01" and (cwin = "01" or cwin = "11")) then -- no cross input or north south cross input or
ignore
        csel<='1';
        crosswalk<="01";
        if(countcross="0110" )then
            crosswalk<= "01";
        end if;
    end if;

    if(c5="0101" and (cew="00" or cwin="01" or cwin="11")) then
        ns<=ewy;
    else
        ns<=cs;
    end if;
when ewy =>--easy west yellow

```

```

--outputs of this state
northsouth <= "100";--red
eastwest <= "010";--yellow
sel<="01"; --count to 1
cwout<= "10"; --walk in ew
if(c1="0001") then
    ns <= ewr;
end if;
when ewr =>--east west red
    --outputs of this state
    northsouth <= "100";--red
    eastwest <= "100";--red
    sel<="01"; --count to 1
    cwout<= "00";---no walking
    if(c1="0001" and turn ='1') then
        ns <= tg;
    elsif(c1="0001" and (turn ='0' or cwin="10" or cwin="11"))then
        ns<=nsg;
    end if;
when tg =>--turn green
    --outputs of this state
    turnsig<= "10"; --turnsig signal light is green
    northsouth <= "100";--red
    eastwest <= "100";--red
    sel<="10"; --count to 5
    cwout<= "00";--no walking
    if(c5="0101")then
        ns <= ty;
    else
        ns<= cs;
    end if;
when ty =>--turn yellow
    --outputs of this state
    turnsig <="01"; --turnsig signal light is yellow
    northsouth <= "100";--red
    eastwest <= "100";--red
    sel<="01"; --count to 1
    cwout<= "00"; --no walking
    if(c1="0001") then
        ns <= nsg;
    else
        ns<=cs;
    end if;

end case;
end process;
end Beh;

```

Counter

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
use ieee.std_logic_unsigned.all;
```

entity counter is

```
Port (clk,reset:in std_logic;
      input:in std_logic_vector(1 downto 0);
      crosser : in std_logic;--person needs to cross street
      c1,c5, crossOut :out std_logic_vector(3 downto 0));--count to 1 and count to 5
end counter;
```

architecture Behavioral of counter is

```
signal tmp1,tmp2, crossertemp : std_logic_vector(3 downto 0);--counter signals

begin

process(reset,clk)
begin
tmp1<="0000";
tmp2<="0000";
crossertemp<="0000";
if(reset='1')then
--reset counts
tmp1<="0000";
tmp2<="0000";
elsif(clk'event and (clk='1'))then--on the rising edge
if(input = "01")then
if(tmp1 < 2) then --count to 1 (0,1)
tmp1 <= tmp1 + "0001";
end if;
elsif(input="10")then
if(tmp2 < 5)then --count to 5 (0,1,2,3,4)
tmp2 <= tmp2 + "0001";
end if;
end if;
if(crosser = '1')then
if(crossertemp<6)then
crossertemp<= crossertemp + "0001";
end if;
end if;
end if;
--set the values
c1 <= tmp1;
c5 <=tmp2;
crossOut <= crossertemp;
end process;
end Behavioral;
```

Seven Segment Display

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
use ieee.std_logic_unsigned.all;
```



```
entity sevSeg is
  Port (input: in std_logic_vector (3 downto 0);
        output: out std_logic_vector(6 downto 0));-- lsb
end ;
```

architecture Behavioral of sevSeg is

```
begin
process(input)
begin
case input is
when "0000" =>
    output <= "1000000"; --0
when "0001" =>
    output <= "1111001"; --1
when "0010" =>
    output <= "0100100";--2
when "0011" =>
    output <= "0110000"; --3
when "0100" =>
    output <= "0011001"; --4
when "0101" =>
    output <= "0010010";--5
when "0110" =>
    output <= "0000010";--6
when "0111" =>
    output <= "1111000";--7
when "1000" =>
    output <= "0000000";--8
when "1001" =>
    output <= "0010000";--9
when "1010" =>
    output <= "0100000";--10 A
when "1011" =>
    output <= "0000011";--11 B
when "1100" =>
    output <= "1000110";--12 C
when "1101" =>
    output <= "0100001";--13 D
when "1110" =>
    output <= "0000110";--14 E
when "1111" =>
    output <= "0001110";--15 F
end case;
end process;

end Behavioral;
```

Constraints

```
set_property IOSTANDARD LVCMOS33 [get_ports {CarEastWest[1]}]  
set_property IOSTANDARD LVCMOS33 [get_ports {CarEastWest[0]}]  
set_property IOSTANDARD LVCMOS33 [get_ports {ew[2]}]
```

```
set_property IOSTANDARD LVCMOS33 [get_ports {ew[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {ew[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {ns[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {ns[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {ns[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {turnout[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {turnout[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports clock]
set_property IOSTANDARD LVCMOS33 [get_ports clockout]
set_property IOSTANDARD LVCMOS33 [get_ports r]
set_property PACKAGE_PIN L1 [get_ports {ew[2]}]
set_property PACKAGE_PIN P1 [get_ports {ew[1]}]
set_property PACKAGE_PIN N3 [get_ports {ew[0]}]
set_property PACKAGE_PIN V19 [get_ports {ns[2]}]
set_property PACKAGE_PIN U19 [get_ports {ns[1]}]
set_property PACKAGE_PIN E19 [get_ports {ns[0]}]
set_property PACKAGE_PIN V3 [get_ports clockout]
set_property PACKAGE_PIN W5 [get_ports clock]
set_property PACKAGE_PIN V14 [get_ports {turnout[1]}]
set_property PACKAGE_PIN U14 [get_ports {turnout[0]}]
set_property PACKAGE_PIN R2 [get_ports {CarEastWest[1]}]
set_property PACKAGE_PIN U1 [get_ports r]
```

```
set_property IOSTANDARD LVCMOS33 [get_ports {cwout[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {cwout[0]}]
set_property PACKAGE_PIN P3 [get_ports {cwout[1]}]
set_property PACKAGE_PIN U16 [get_ports {cwout[0]}]
```

```
set_property PACKAGE_PIN T1 [get_ports {CarEastWest[0]}]
```

```
set_property IOSTANDARD LVCMOS33 [get_ports {seven[6]}]
set_property IOSTANDARD LVCMOS33 [get_ports {seven[5]}]
set_property IOSTANDARD LVCMOS33 [get_ports {seven[4]}]
set_property IOSTANDARD LVCMOS33 [get_ports {seven[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {seven[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {seven[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {seven[0]}]
set_property PACKAGE_PIN W7 [get_ports {seven[6]}]
set_property PACKAGE_PIN W6 [get_ports {seven[5]}]
set_property PACKAGE_PIN U8 [get_ports {seven[4]}]
set_property PACKAGE_PIN V8 [get_ports {seven[3]}]
set_property PACKAGE_PIN U5 [get_ports {seven[2]}]
set_property PACKAGE_PIN V5 [get_ports {seven[1]}]
set_property PACKAGE_PIN U7 [get_ports {seven[0]}]
set_property PACKAGE_PIN W2 [get_ports {walk[1]}]
```

```
set_property PACKAGE_PIN R3 [get_ports {walk[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {walk[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {walk[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports turn]
```

```
set_property PACKAGE_PIN V7 [get_ports turn]
```